

Lect 14**Binary Multiplier****CS221: Digital Design**

Dr. A. Sahu
Dept of Comp. Sc. & Engg.
Indian Institute of Technology Guwahati

1

Outline

- Array Binary Multiplier
- Sequential Multiplier
- High Radix Multiplier
- Booth Multiplier
- Programmable logic Device (PLD)
 - PLA, PAL, ROM, GAL, CPLD, CLB
 - SoftwareHDLs

2


Delay of Adder

- Ripple Carry Adder (RCA) = $N * T_c = \alpha N$
- Manchester RCA = $N * T_m = \alpha N$
- Carry Skip Adder
Total Delay = $p (N/m) T_s + (p-1) * (N/m) * m * T_c$
 $T = N * (p/m * T_s + (p-1) T_c) = \alpha N$
- Carry Select Adder = Independent of Data
Delay of select = T_s
 $T = (N/m - 1) T_s + m T_c$
 $T = N * T_s / m + (m T_c - T_s) = \alpha N + c$
- CLA : $\log_4 N$, Area:
 $O(N) = O(N/4 + N/16 + \dots) * A_{cla_4} = O(N/3) * A_{cla_4}$


4

**Efficient
Multiplier Design****Multiplication: paper - pencil method**


A	0	1	1				
B	1	0	1				
	0	1	1		0	0	0
	0	0	0	x	0	0	0
	0	1	1	x	0	0	0
AxB	0	1	1	1	1	1	1

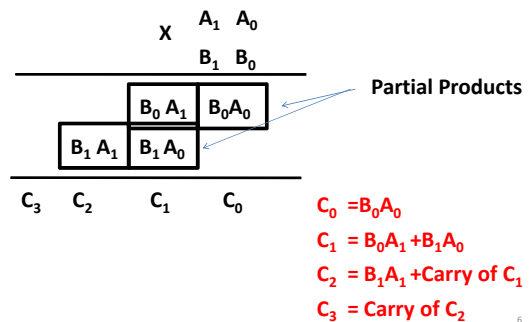Binary Multiplier: 2 Bits

Binary Multiplier: 2 Bits

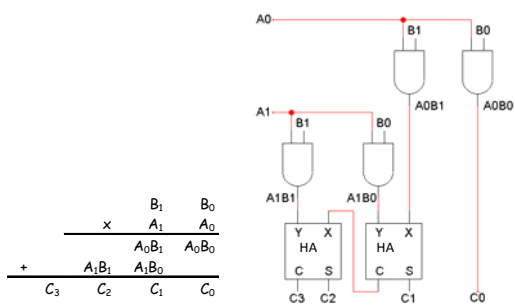

Binary Multiplier: 4 Bits

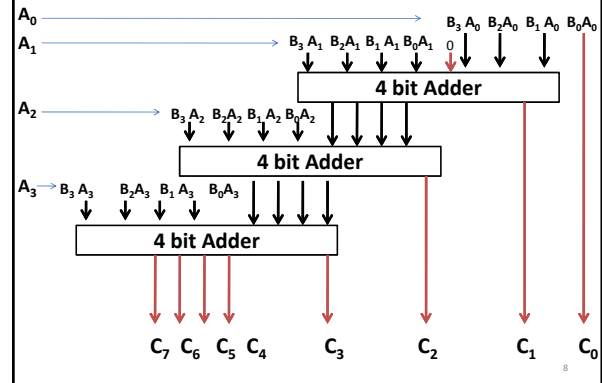

Simple Speeding up

$$A \times B = \sum_{i=0}^{n-1} A \cdot B_i \times 2^i = \sum_{i=0}^{n-1} T_i$$

$$= A \cdot B_0 \times 2^0 + A \cdot B_1 \times 2^1 + \dots + A \cdot B_{n-1} \times 2^{n-1}$$

- **Assumption: Generate All the term in parallel**
- N Addition can be done in parallel in Log(N) steps using N/2 Adder.
- **Adder complexity is Linear O(N) using RCA**
 - Area : Number of Adder*Area Per Adder = N/2 * N
 - Delay : Delay per Adder* Steps = N. lg N
- **Adder complexity CLA Log (N)**
 - Area : Number of Adder*Area Per Adder = N/2 * 2N
 - Delay : Delay per Adder* Steps = lg N. lg N = (lg N)²

Algorithm Serial Multiplication: D & C

- To multiply two n-digit integers:
 - Multiply **four** ½n-digit integers.
 - Add two ½n-digit integers, and shift to obtain result.

$$x = 2^{n/2} \cdot x_1 + x_0$$

$$y = 2^{n/2} \cdot y_1 + y_0$$

$$xy = (2^{n/2} \cdot x_1 + x_0)(2^{n/2} \cdot y_1 + y_0) = 2^n \cdot x_1 y_1 + 2^{n/2} \cdot (x_1 y_0 + x_0 y_1) + x_0 y_0$$

$$T(n) = \underbrace{4T(n/2)}_{\text{recursive calls}} + \underbrace{\Theta(n)}_{\text{add, shift}} \Rightarrow T(n) = \Theta(n^2)$$

Improved: Karatsuba Multiplication

- To multiply two n-digit integers:
 - Add two ½n digit integers.
 - Multiply **three** ½n-digit integers. (Re use of Term)

$$x = 2^{n/2} \cdot x_1 + x_0$$

$$y = 2^{n/2} \cdot y_1 + y_0$$


$$xy = 2^n \cdot x_1 y_1 + 2^{n/2} \cdot (x_1 y_0 + x_0 y_1) + x_0 y_0$$

$$= 2^n \cdot x_1 y_1 + 2^{n/2} \cdot ((x_1 + x_0)(y_1 + y_0) - x_1 y_1 - x_0 y_0) + x_0 y_0$$

$$T(n) = \underbrace{3T(n/2)}_{\text{recursive calls}} + \underbrace{\Theta(n)}_{\text{add, shift}} \Rightarrow T(n) = \Theta(n^{\log_2 3}) = \Theta(n^{1.58})$$

N bit Multiplication: FFT Method

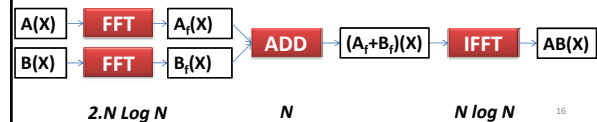- Idea: $1024 \cdot 16 = 2^{10} \cdot 2^4 = 2^{10+4} = 2^{14} = 16384$
- FFT based multiplication
 - N Bit binary numbers $A(X) = A_{n-1}2^{n-1} + A_{n-2}2^{n-2} + \dots + A_0 \cdot 1$
 - Polynomial multiplication $A(X) * B(X)$
 - $A(X) * B(X) = \text{IFFT}(\text{FFT}(A(X)) + \text{FFT}(B(X)))$
 - Complexity : $2n \lg n + n + n \lg n = O(n \lg n)$




Shift add multiplier (sequential)


$$A \times B = \sum_{i=0}^{n-1} A \cdot B_i \times 2^i$$

step1: i=0; s=0 do { step2: s += A · B _i × 2 ⁱ i ++ } while (i < n)	step1: i=0; s=0 do { step2: if (B _i) s += A A = 2xA i ++ } while (i < n)	step1: i=0; s=0 do { step2: if (B ₀) s += A A = 2xA B = B/2; i ++ } while (i < n)
----------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------


Sequential shift add multiplier 1

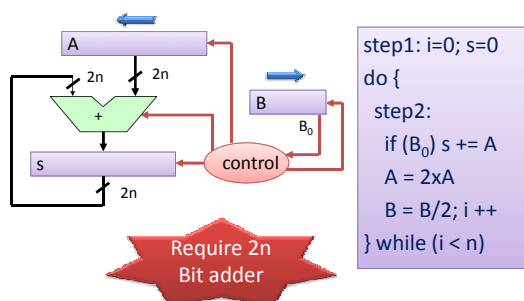

Sequential shift add multiplier 2

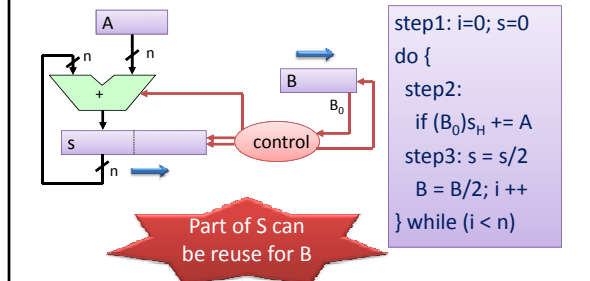


Sequential shift add multiplier 3

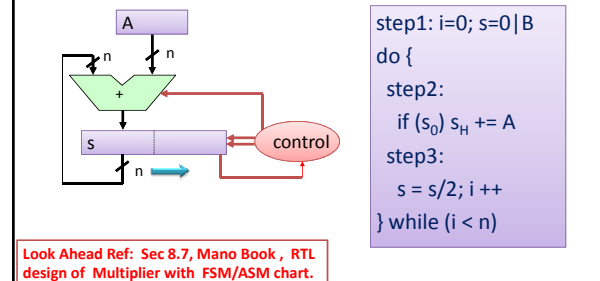


Higher Radix Multiplication

21

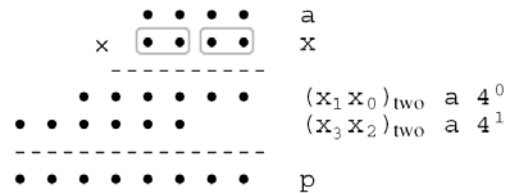Radix-4, or two-bit-at-a-time, multiplication in dot notation



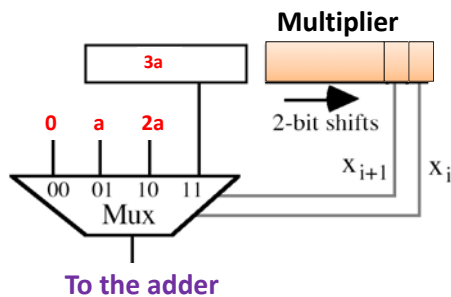Multiple generation part of a radix-4 multiplier with precomputation of $3a$



Higher Radix Multiplication

- In radix-8, one must precompute $3a, 5a, 7a$
– Overhead becomes prohibitive and does not help

Higher Radix Multiplication Booth Encoding

25

Radix-2 Booth Recoding

$\begin{matrix} & j+1 & j & i \\ 1 & 0 & 0 & 1 & 1 & 1 & 0 & 1 & 0 & 1 & 1 & 1 & 0 & \text{Operand } x \\ (1) & -1 & 0 & 1 & 0 & 0 & -1 & 1 & 0 & -1 & 1 & -1 & 1 & 0 & 0 & -1 & 0 & \text{Recoded version } y \end{matrix}$

Justification

$$2^j + 2^{j-1} + \dots + 2^{i+1} + 2^i = 2^{i+1} - 2^j$$

Radix-2 Booth Recoding

x_i	x_{i-1}	y_i	Explanation
0	0	0	No string of 1s in sight
0	1	1	End of string of 1s in x
1	0	-1	Beginning of string of 1s in x
1	1	0	Continuation of string of 1s in x

$\begin{matrix} 1 & 0 & 0 & 1 & 1 & 1 & 0 & 1 & 0 & 1 & 1 & 1 & 0 & \text{Operand } x \\ (1) & -1 & 0 & 1 & 0 & 0 & -1 & 1 & 1 & -1 & 1 & -1 & 1 & 0 & 0 & -1 & 0 & \text{Recoded version } y \end{matrix}$

$$y_i = -x_i + x_{i-1}$$

Radix-2 Booth Multiplier Basic Step

