

CS221: Digital Design

<http://jatinga.iitg.ernet.in/~asahu/cs221>

FSM: Examples, Optimization and State Encoding

A. Sahu

Dept of Comp. Sc. & Engg.


Indian Institute of Technology Guwahati

Outline

- FSM Examples
- Moore Vs Mealy Machines
- FSM State Optimization : RM and IC
- FSM State Encoding
- FSM + Data Path
- ASM

FSM Example 5 : Code Detector

 
- Unlock door ($u=1$) only when buttons pressed in sequence:
 - **start, then red, blue, green, red**
- Input from each button: s, r, g, b
 - Also, output a indicates that some colored button pressed



FSM Example 5: Code Detector

- Wait for start ($s=1$) in “Wait”,
- **Once started (“Start”)**
 - If see red, go to “Red1”
 - Then, if see blue, go to “Blue”, Then, if see green, go to “Green”, Then, if see red, go to “Red2”
 - In that state, open the door ($u=1$)
 - Wrong button at any step, return to “Wait”


FSM Example 5 : Code Detector

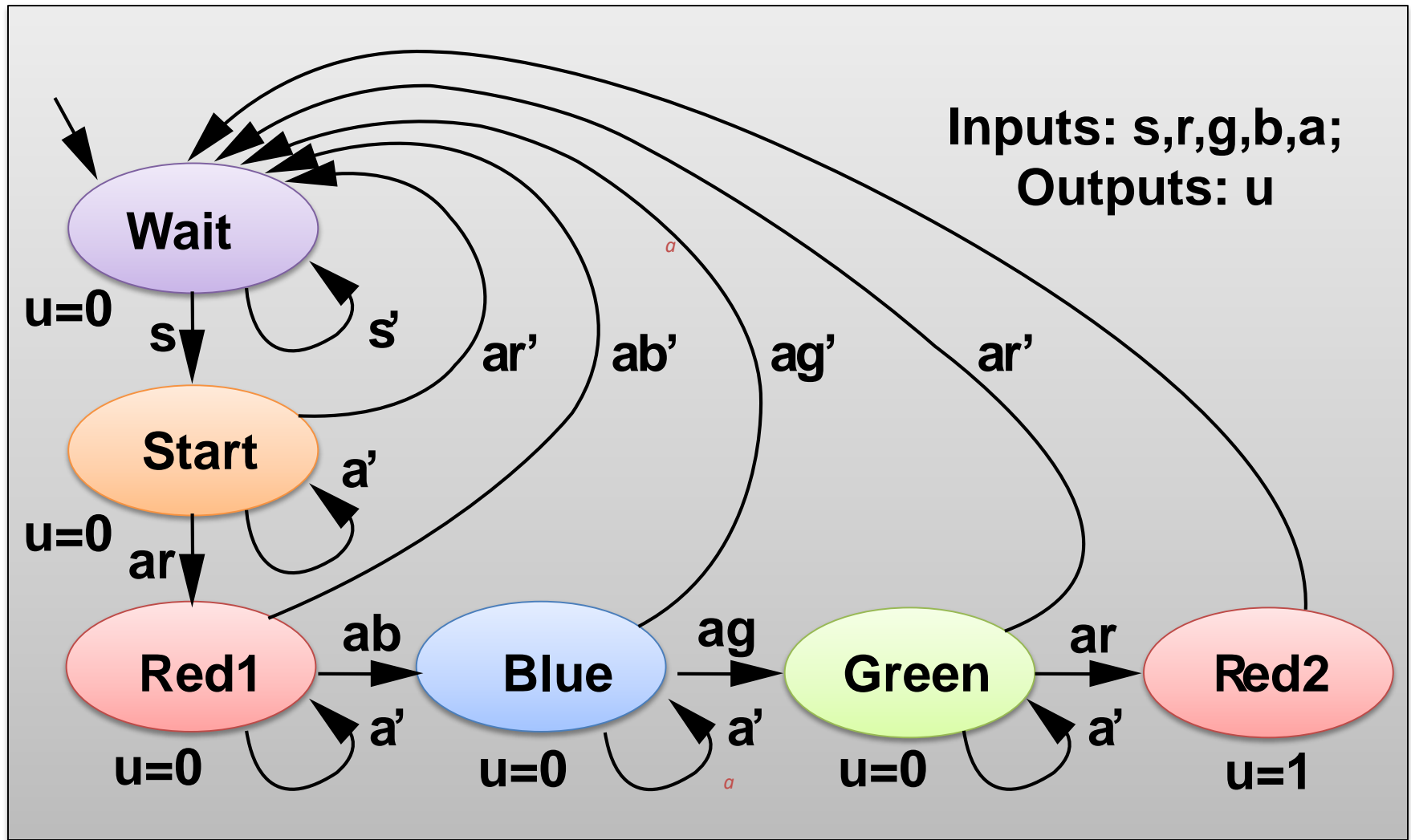

Q: Can you trick this FSM to open the door, without knowing the code?

A: Yes, hold all buttons simultaneously


Improve FSM for Code Detector

 


- **New transition conditions** detect if wrong button pressed, returns to “Wait”
- FSM provides formal, concrete means to accurately define desired behavior

Common Pitfalls Regarding Transition Properties

 - *Only* one condition should be true
 - For all transitions leaving a state
 - Else, which one?




$ab=11$ –
next state?

 


Common Pitfalls Regarding Transition Properties

 - *One* condition must be true
 - For all transitions leaving a state
 - Else, where go?




what if
 $ab=00$?

 

Verifying Correct Transition Properties

 - Can verify using Boolean algebra
 - Only one condition true: AND of each condition pair (for transitions leaving a state) should equal 0
 - \rightarrow proves pair can never simultaneously be true
 - Example




Answer:

$$\begin{aligned} & a * a'b \\ &= (a * a') * b \\ &= 0 * b \\ &= 0 \\ &\text{OK!} \end{aligned}$$

Verifying Correct Transition Properties

 - Can verify using Boolean algebra
 - One condition true: OR of all conditions of transitions leaving a state) should equal 1
 - \rightarrow proves at least one condition must be true
 - Example



$$\begin{aligned} & a + a'b \\ &= a*(1+b) + a'b \\ &= a + ab + a'b \\ &= a + (a+a')b \\ &= a + b \end{aligned}$$

Fails! Might not be 1 (i.e., $a=0, b=0$)


Verifying Correct Transition Properties

- Can verify using Boolean algebra
 - Only one condition true
 - One condition true

a


Q: For shown transitions, prove whether:

 - * Only one condition true (AND of each pair is always 0)
- * One condition true (OR of all transitions is always 1)




$$a + a'b + a'b' = 1$$

Evidence that Pitfall is Common

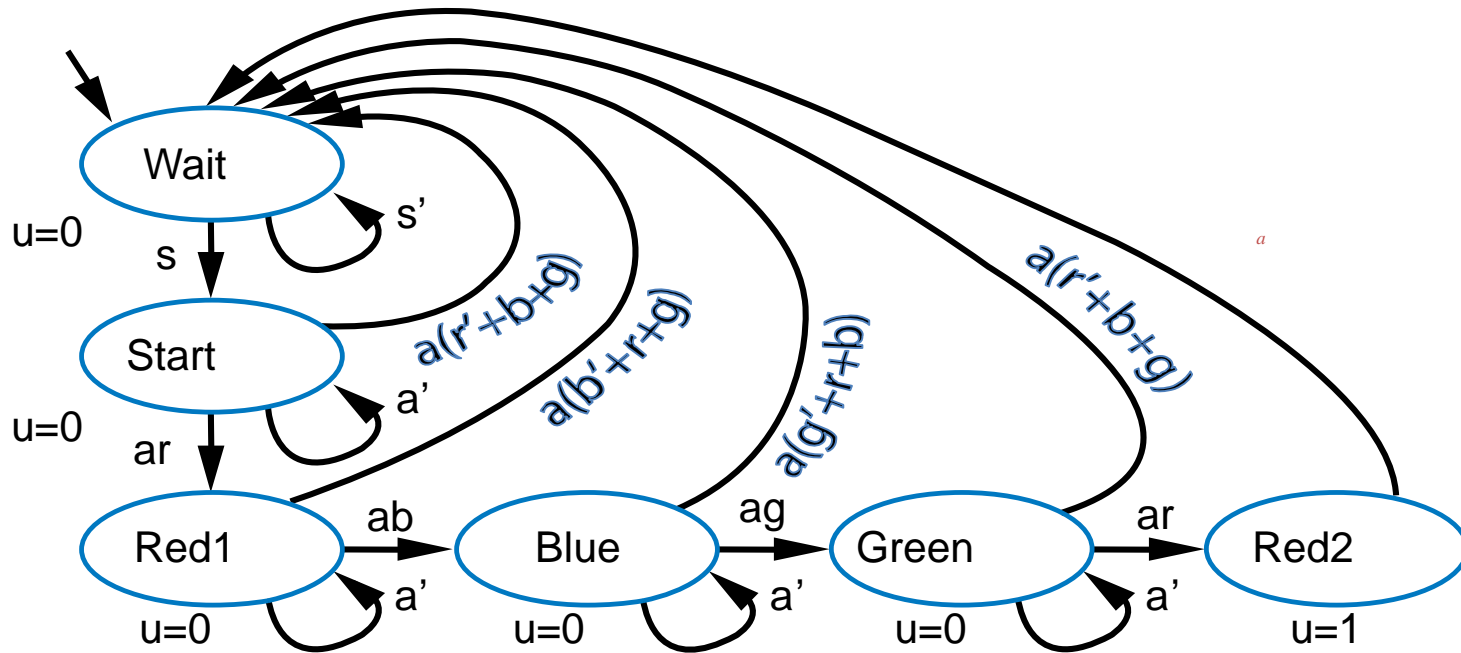

- Recall code detector FSM
 - We “fixed” a problem with the transition conditions
 - Do the transitions obey the two required transition properties?

Evidence that Pitfall is Common

 

Consider transitions of state *Start*, and “only one true” property


$$\begin{aligned} & ar * a' \\ &= (a * a')r \\ &= 0 \end{aligned}$$

$$\begin{aligned} & a' * a(r'+b+g) \\ &= 0 * r \\ &= 0 \end{aligned}$$

$$\begin{aligned} & ar * a(r'+b+g) \\ &= (a' * a) * (r' + b + g) = 0 * (r' + b + g) \\ &= (a * a) * r * (r' + b + g) = * r * (r' + b + g) \\ &= arr' + arb + arg \\ &= 0 + arb + arg \\ &= arb + arg \\ &= ar(b+g) \quad // \text{ not ZERO} \end{aligned}$$

Fails! Means that two of Start's transitions could be true

Evidence that Pitfall is Common

 

Consider transitions of state *Start*, and “only one true” property

Intuitively: press red and blue buttons at same time: conditions ar , and $a(r'+b+g)$ will both be true. Which one should be taken?

Q: How to solve?

A: ar should be $arb'g'$
(likewise for ab , ag , ar)

$$arb'g' * a(r'+b+g) = 0$$

FSM Types

- Two main types of FSMs
 - Moore FSM : output is only function of state
 - Mealy FSM: output is function of state and inputs

Set Theoretic Description

Moore Machine is an ordered quintuple

$$M = (S, I, O, \delta, \lambda)$$

where

S = Finite set of states $\neq \Phi, \{s_1, s_2, \dots, s_n\}$

I = Finite set of inputs $\neq \Phi, \{i_1, i_2, \dots, i_m\}$

O = Finite set of outputs $\neq \Phi, \{o_1, o_2, \dots, o_l\}$

δ = Next state function which maps $S \times I \rightarrow S$

λ = Output function which maps $S \rightarrow O$

Set Theoretic Description

Mealy Machine is an ordered quintuple

$$\text{Mealy} = (\mathbf{S}, \mathbf{I}, \mathbf{O}, \delta, \beta)$$

where

\mathbf{S} = Finite set of states $\neq \Phi, \{s_1, s_2, \dots, s_n\}$

\mathbf{I} = Finite set of inputs $\neq \Phi, \{i_1, i_2, \dots, i_m\}$

\mathbf{O} = Finite set of outputs $\neq \Phi, \{o_1, o_2, \dots, o_l\}$

δ = Next state function which maps $\mathbf{S} \times \mathbf{I} \rightarrow \mathbf{S}$

β = Output function which maps $\mathbf{S} \times \mathbf{I} \rightarrow \mathbf{O}$

Clocked synchronous FSM


- **Clocked**
 - All storage elements employ a clock input (i.e. all storage elements are flip-flops)
- **Synchronous**
 - All of the flip flops use the same clock signal

Clocked synchronous FSM


- **FSM**
 - State machine is simply another name for sequential circuits. Finite refers to the fact that the number of states the circuit can assume is finite
- **Async FSM:** A synchronous clocked FSM changes state only when a triggering edge (or tick) occurs on the clock signal

Clocked synchronous FSM structure

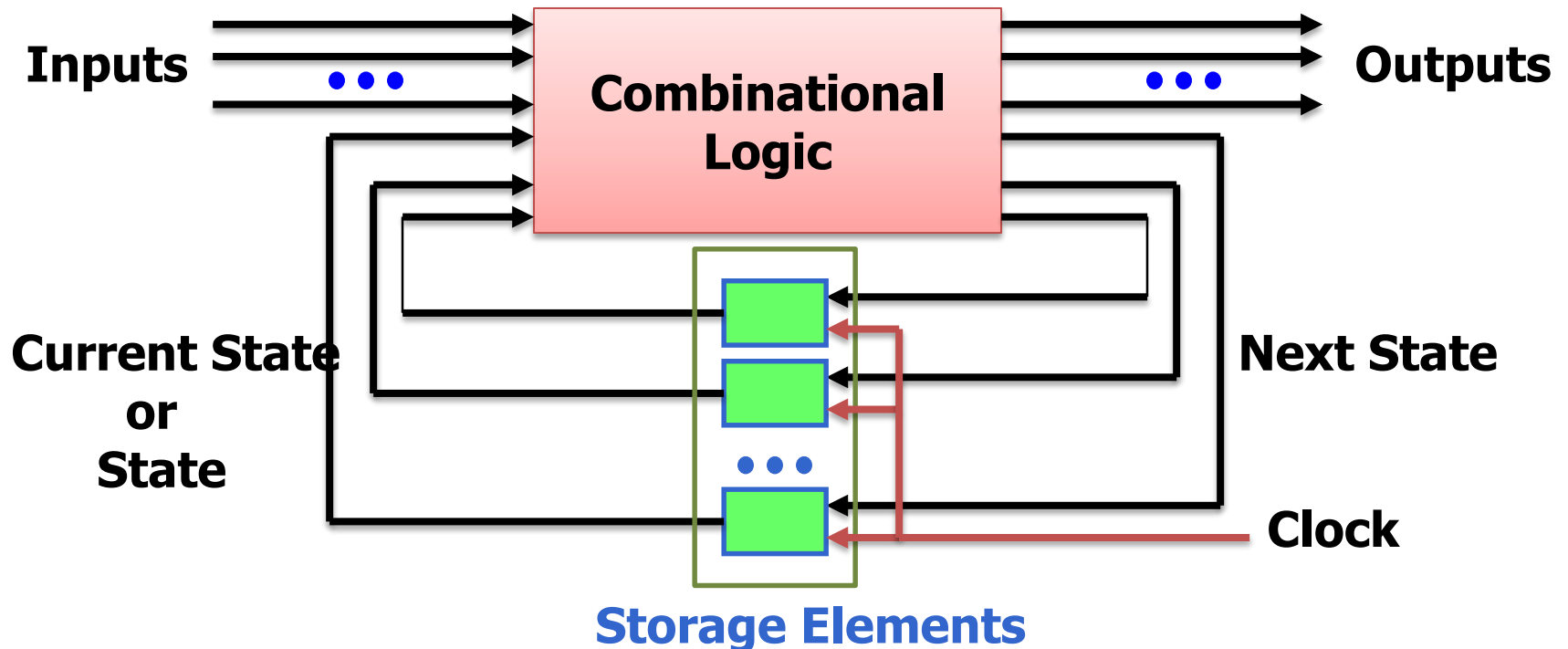- **States:** determined by possible values in sequential storage elements
- **Transitions:** change of state
- **Clock:** controls when state can change by controlling storage elements




Moore machine

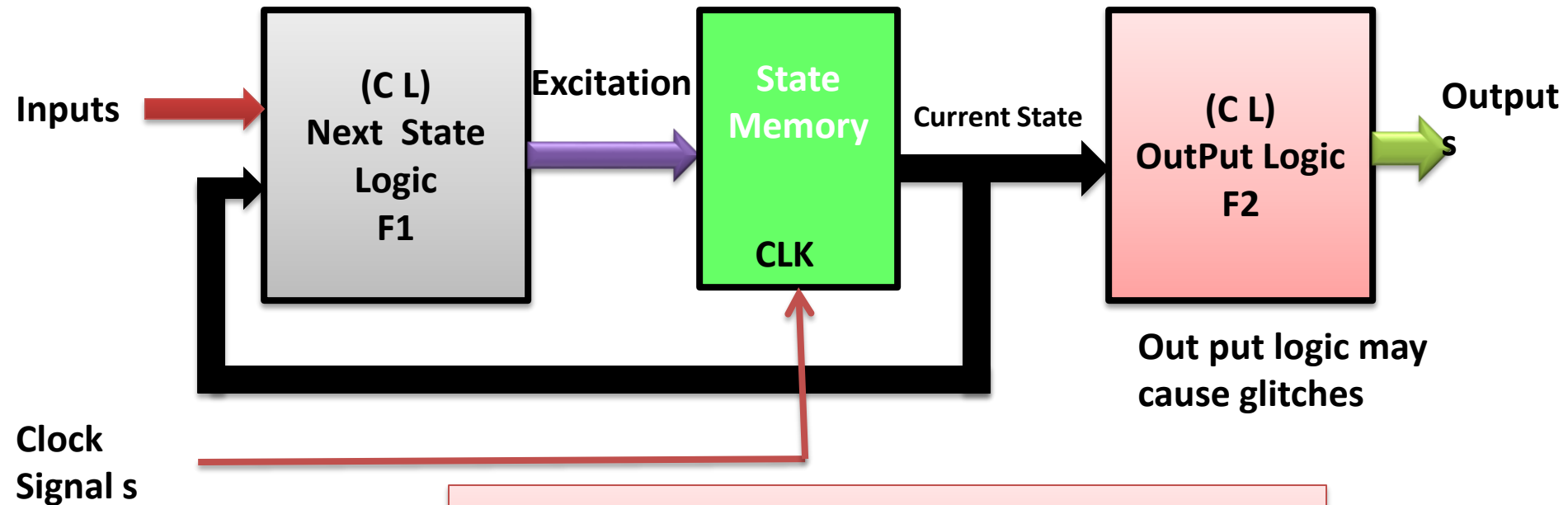

Next state = $F_2(\text{current state, inputs})$
Output = $G_2(\text{current state})$

Mealy machine

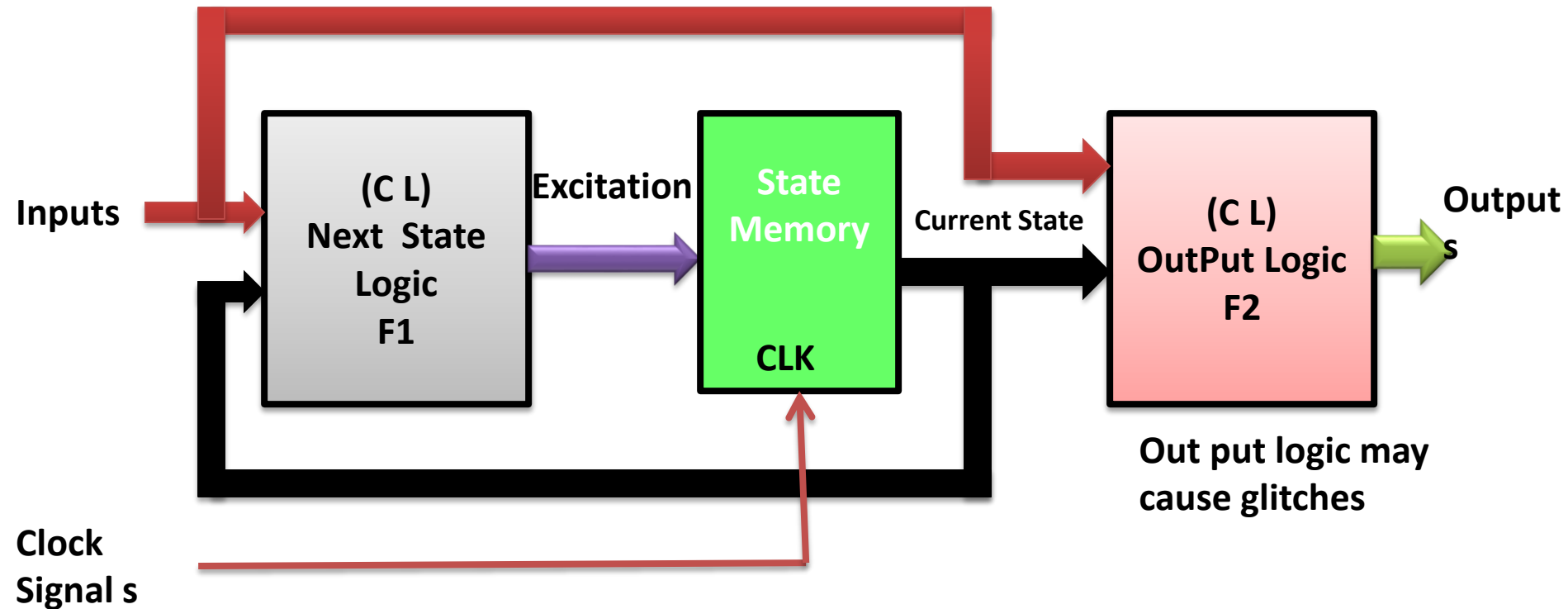- A Much better name of State “Memory” is State Storage




State Storage= Set of n FFs
 2^n State can be stored

Next state = $F_1(\text{current state, inputs})$
Output = $F_2(\text{current state, inputs})$

Example of Moore & Melay Machine


- Parity Checker Solution: (Moore)

 

Moore Machine: Output is associated with the state and hence appears after the state transition take place.



Example of Moore & Mealy Machine

- Parity Checker Solution: (Mealy)

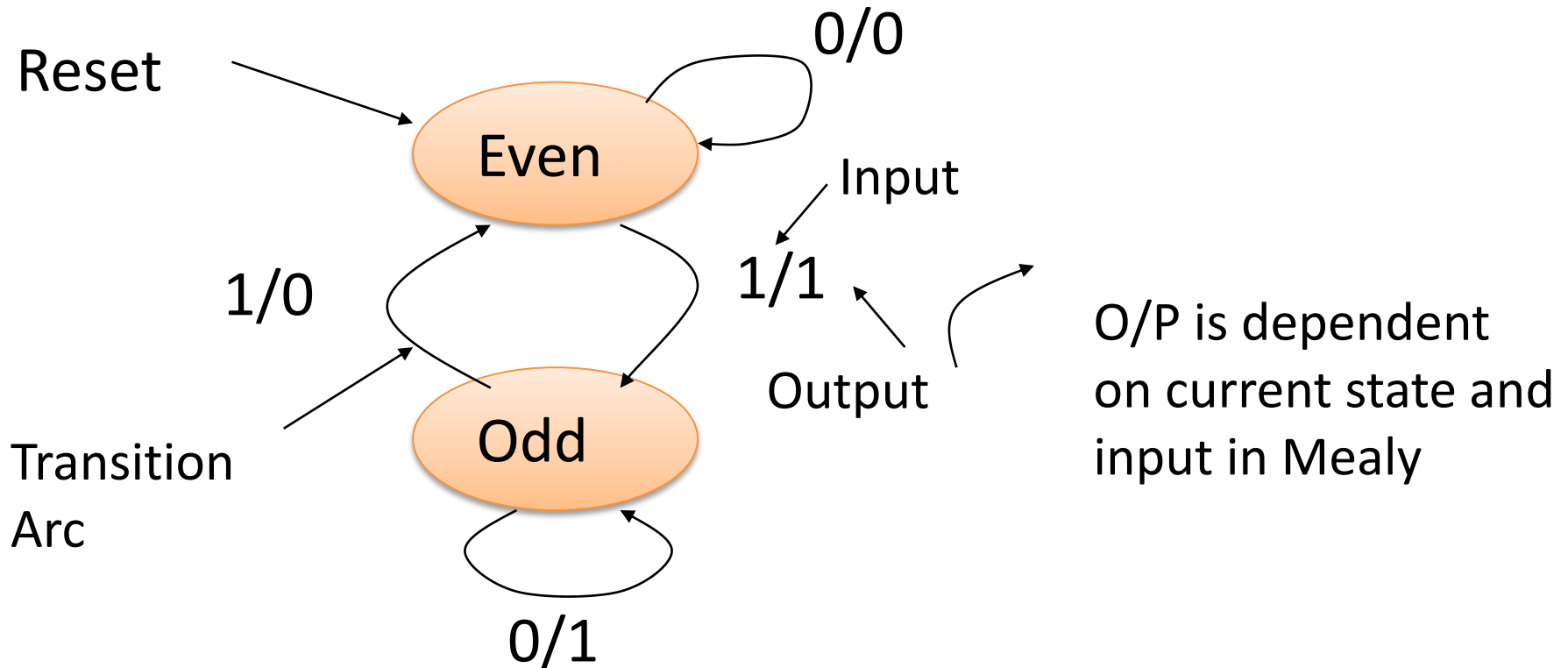


Mealy Machine: Output is associated with the state transition, and appears before the state transition is completed (by the next clock pulse).

Implementation

  


Moore O/P is synchronized with clock.

Parity Checker: Mealy M/C Implementation

 

D-FF

 

T-FF

Mealy O/P is not synchronized with clock.

Comparison : Mealy FSM Vs Moore FSM

- **Mealy** machines have **less states**
 - Outputs are on transitions (n^2) rather than states (n)
- **Moore** machines are **safer** to use
 - Outputs change at clock edge (always one cycle later)
- Mealy machines: input change can cause output change as soon as logic is done
 - A **big problem** when two machines are interconnected
 - Asynchronous feedback **may** occur if one isn't careful

Comparison : Mealy FSM Vs Moore FSM


- **Mealy** machines **react faster** to inputs
 - react in same cycle – don't need to wait for clock
 - outputs **may** be considerably shorter than the clock cycle
 - in Moore machines, more logic **may** be necessary to decode state into outputs – there **may** be more gate delays after clock edge

FSM Example : Mealy vs Moore

- Design a system that outputs a '1' whenever it receives a multiple of 3 # of 1's (i.e., 0, 3, 6, 9, etc. # of 1's) on a serial input line x.

FSM Example: Moore Machine

 
- Design a system that outputs a '1' whenever it receives a multiple of 3 # of 1's (i.e., 0, 3, 6, 9, etc. # of 1's) on a serial input line x.



Moore Machine

FSM Example: Moore Machine

 - Design a system that outputs a '1' whenever it receives a multiple of 3 # of 1's (i.e., 0, 3, 6, 9, etc. # of 1's) on a serial input line x.



Mealy Machine


Mealy Vs Moore : Problem

- $\Sigma_o = \{t, f\}$ $\Sigma_I = \{0, 1\}$
- Outputs $t \Leftrightarrow$ at least 2 last input digits are same

Solutions to Problem

- Mealy implementation
 - Needs only 3 states
- Moore implementation
 - Needs 2 more almost duplicated states just in order to the output value t there.

FSM: Mealy Machine

 

FSM: Moore Machine

Outputs **true** if at least 2 last input digits are same

Is it possible to design Moore
FSM of the same problem with
3 state ?

You can try now..

FSM: Moore Machine

