

**CS221: Digital Design**

**<http://jatinga.iitg.ernet.in/~asahu/cs221>**

# **Finite State Machine**

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

# Outline

- Discussion about Quiz
  - Q1: JK FF, Q2: value just before clock edge,
  - Q3: FSM implementation using D-FF of 3 bit Grey Ctr
  - Q4: FSM of 3 bit Ctr,  $Z_1Z_2Z_3$  are output based on state
  - Q5: FSM of 3 bit Gray Ctr,  $Z_1Z_2Z_3$  are output based on state
- FSM Examples
- FSM of Register and Counter
- Design of Counters using FSM and other FFs

# Outline

- Q3, Q4 and Q5
- Z1: 00101000 00101000 00101000....
- Z2: 11011011 11011011 11011011....
- Z3: 00110111 00110111 00110111....


Grey Code:

CBA	CnBnAn	Z1Z2Z3
000	001	010
001	010	010
010	011	101
011	100	011
100	101	110
101	110	001
110	111	011
111	000	011

CBA	CnBnAn	Z1Z2Z3
000	001	010
001	011	010
010	110	101
011	010	011
100	000	110
101	100	001
110	111	011
111	101	011
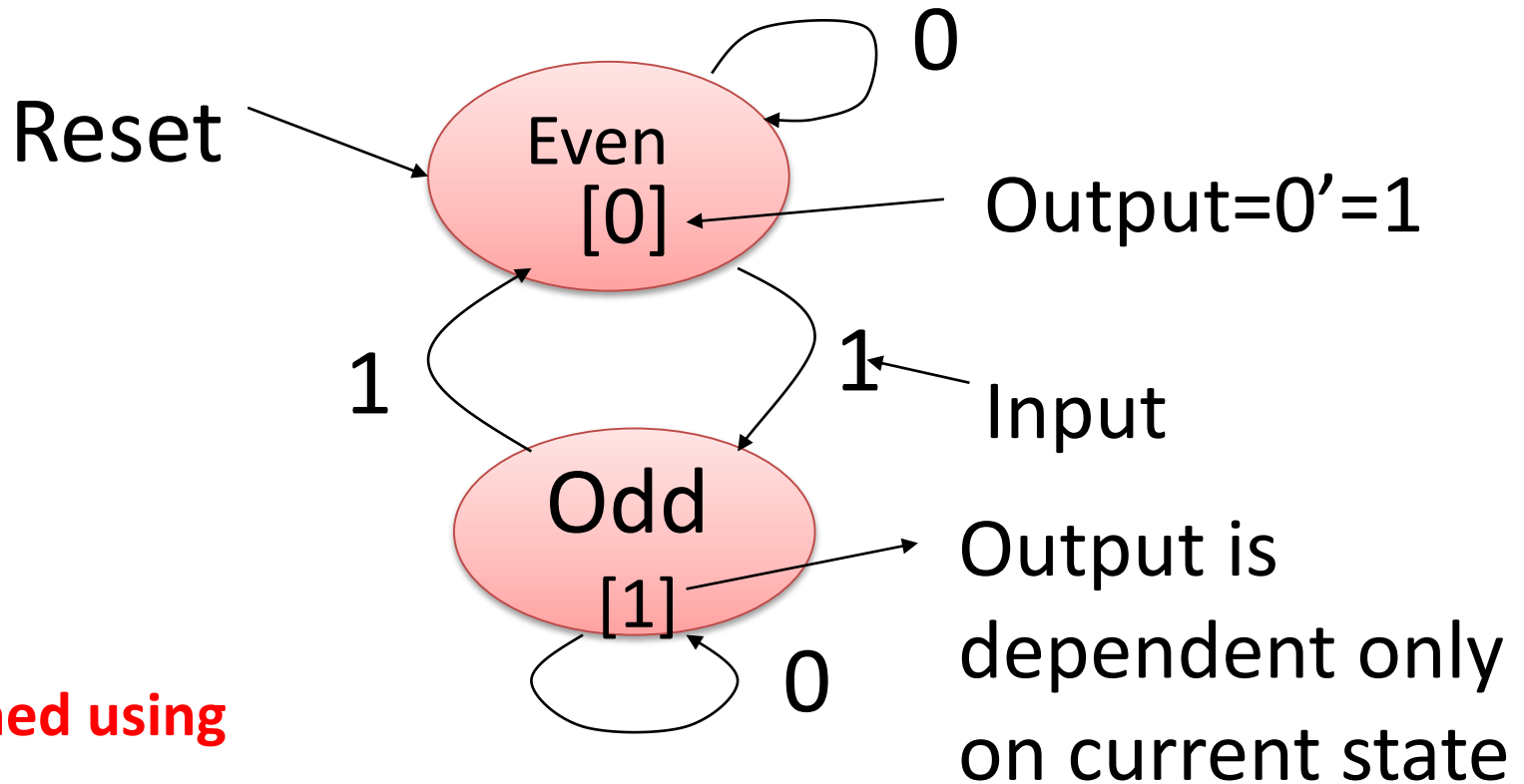
# FSM Example 1: Parity Encoder



- Input: 1 or 0 // entering as stream
- Output: output a 1 when total number of 1 is even



**T- FF :**  
**designed using**  
**D-FF**

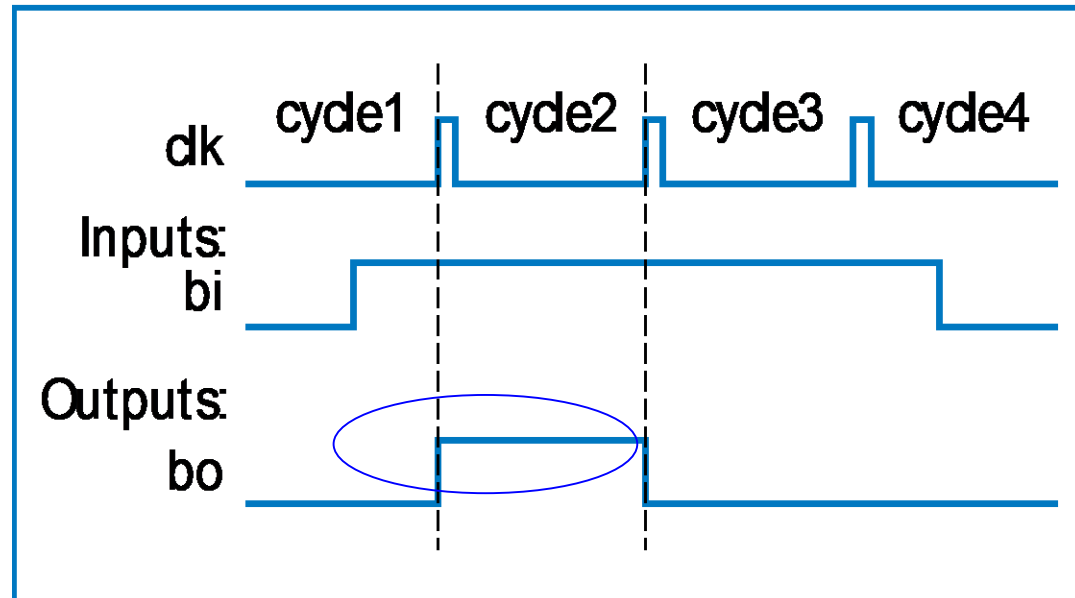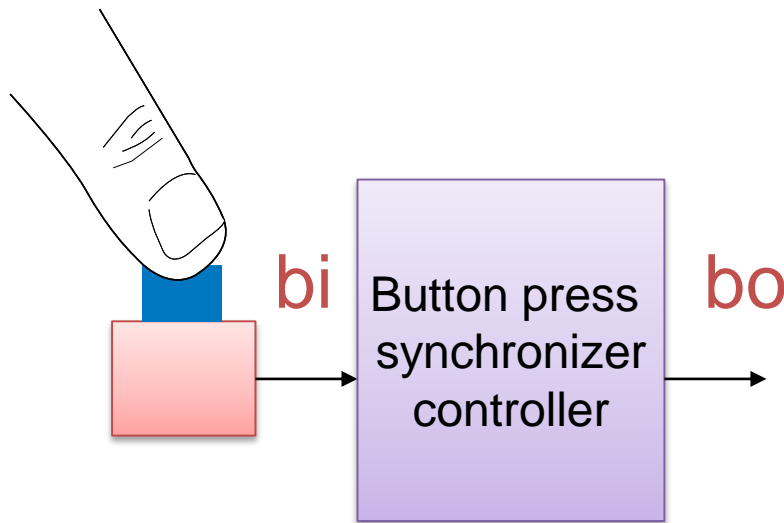
# FSM Example 2 : Button Press Synchronizer

- **English Language Specification**
- We want simple sequential circuit
  - Converts button press to single cycle duration
  - Regardless of length of time that button actually pressed



# FSM Example 2 : Button Press Synchronizer

FSM inputs: bi; FSM outputs: bo

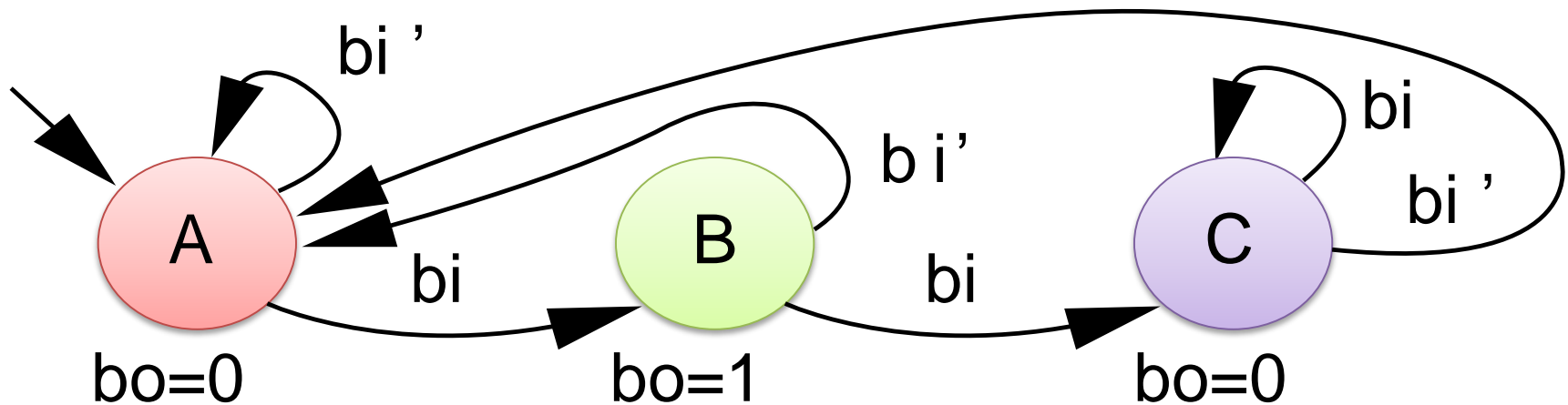

I am Off  
When B=0


I am On in First  
CLK and  
When B=1

I am Off  
Even if B=1

## Step 1: Design FSM

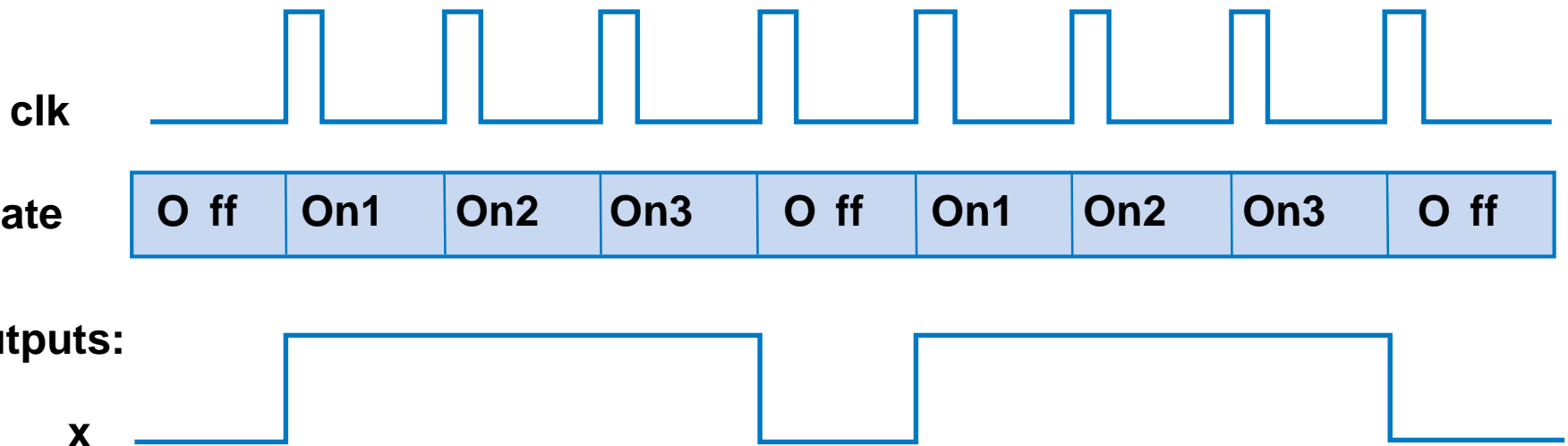
# FSM Example 3: 1: 0,1,1,1,repeat

- Want 0, 1, 1, 1, 0, 1, 1, 1, ...
  - Each value for one clock cycle
- Can describe as FSM: Four states, Transition on rising clock edge to next state


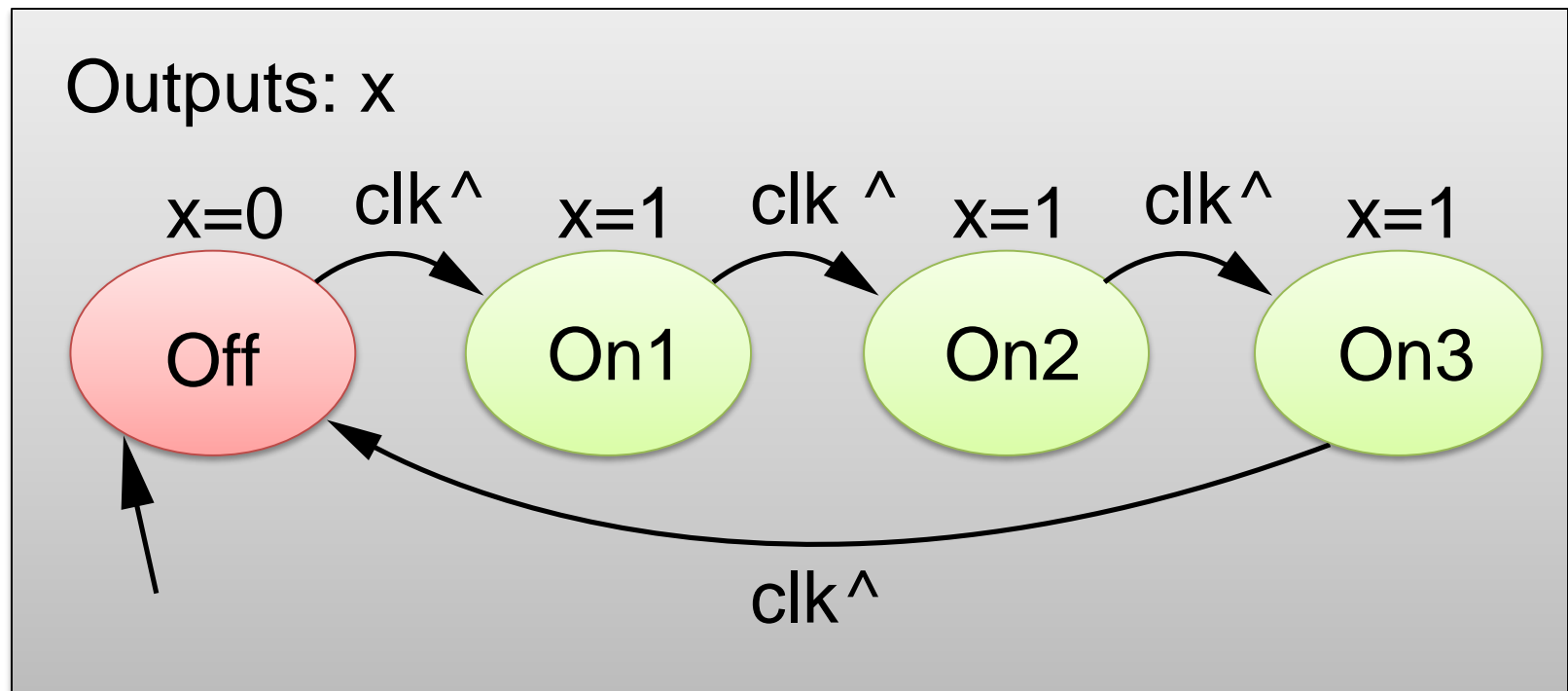
## FSM Example 3: : 0,1,1,1,repeat

- Want 0, 1, 1, 1, 0, 1, 1, 1, ...
  - Each value for one clock cycle
- Can describe as FSM: Four states, Transition on rising clock edge to next state







## FSM Example 4: Three-Cycles High Laser Timer

- Four states: Wait in “Off” state while  $b$  is 0 ( $b'$ )
- When  $b=1$  (& rising clock edge), transition to On1
  - Sets  $X=1$
  - On next two clock edges, transition to On2, then On3, which also set  $x=1$
- So  $x=1$  for three cycles after button pressed
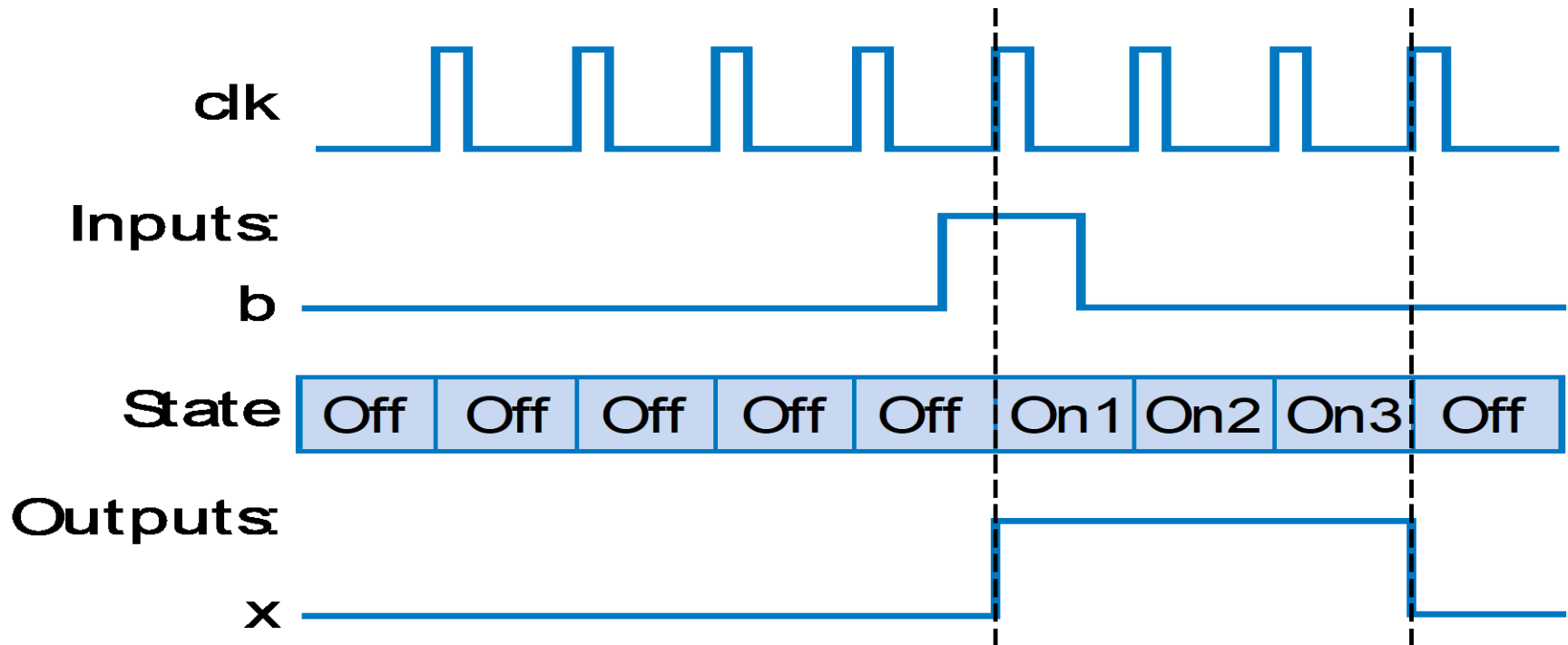
# FSM Example 4 : Three-Cycles High Laser Timer


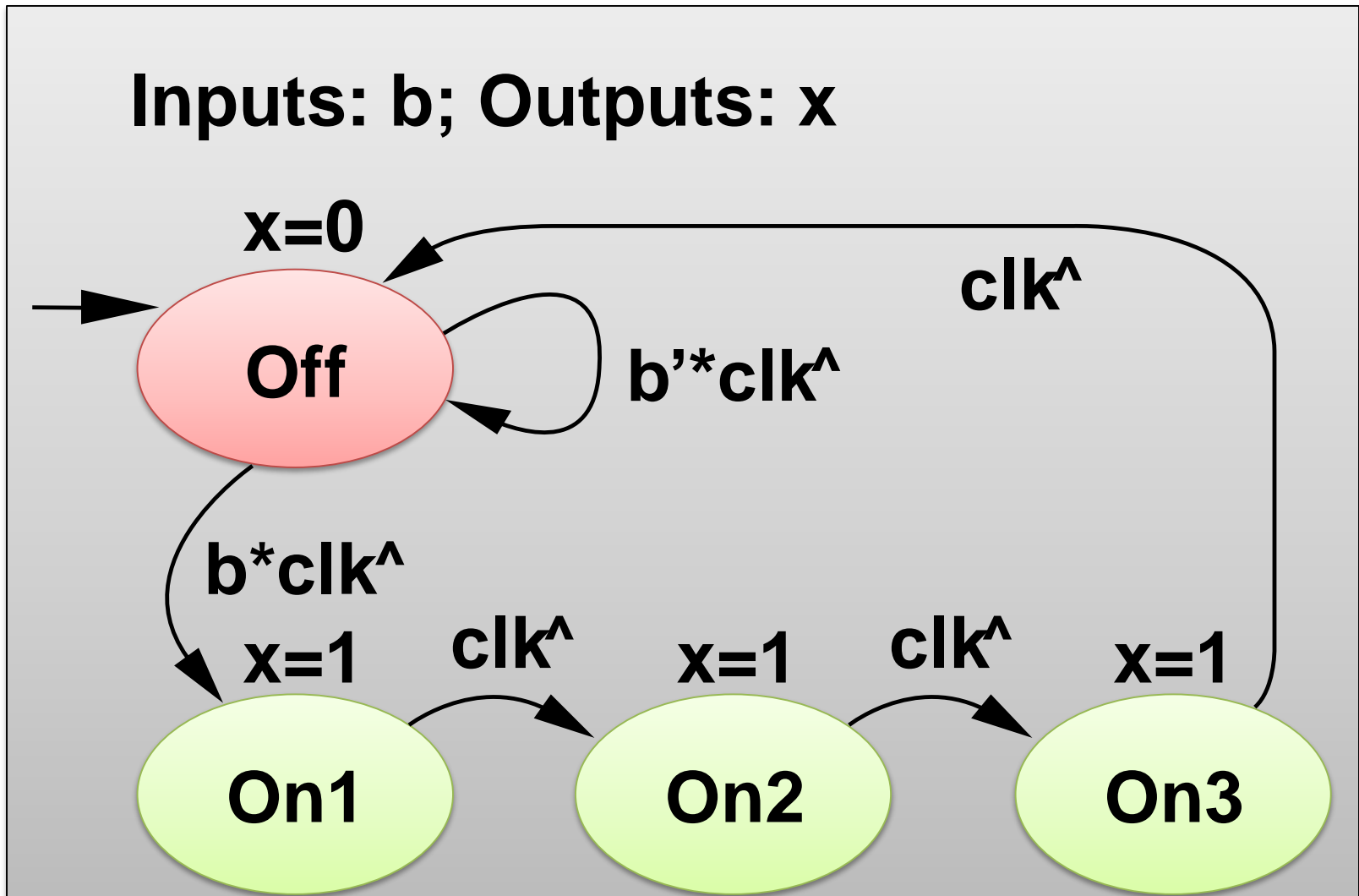
## FSM Example 4 : Three-Cycles High Laser Timer




## FSM Example 4 : Three-Cycles High Laser Timer

- Showing rising clock on every transition: cluttered
- Make implicit -- assume every edge has rising clock
- What if we wanted a transition *without* a rising edge
  - Asynchronous FSMs -- less common, and advanced topic
  - We consider *synchronous* FSMs
  - **All transition on rising edge**

# FSM Simplification: Rising Clock Edges Implicit


Inputs:  $b$ ; Outputs:  $x$

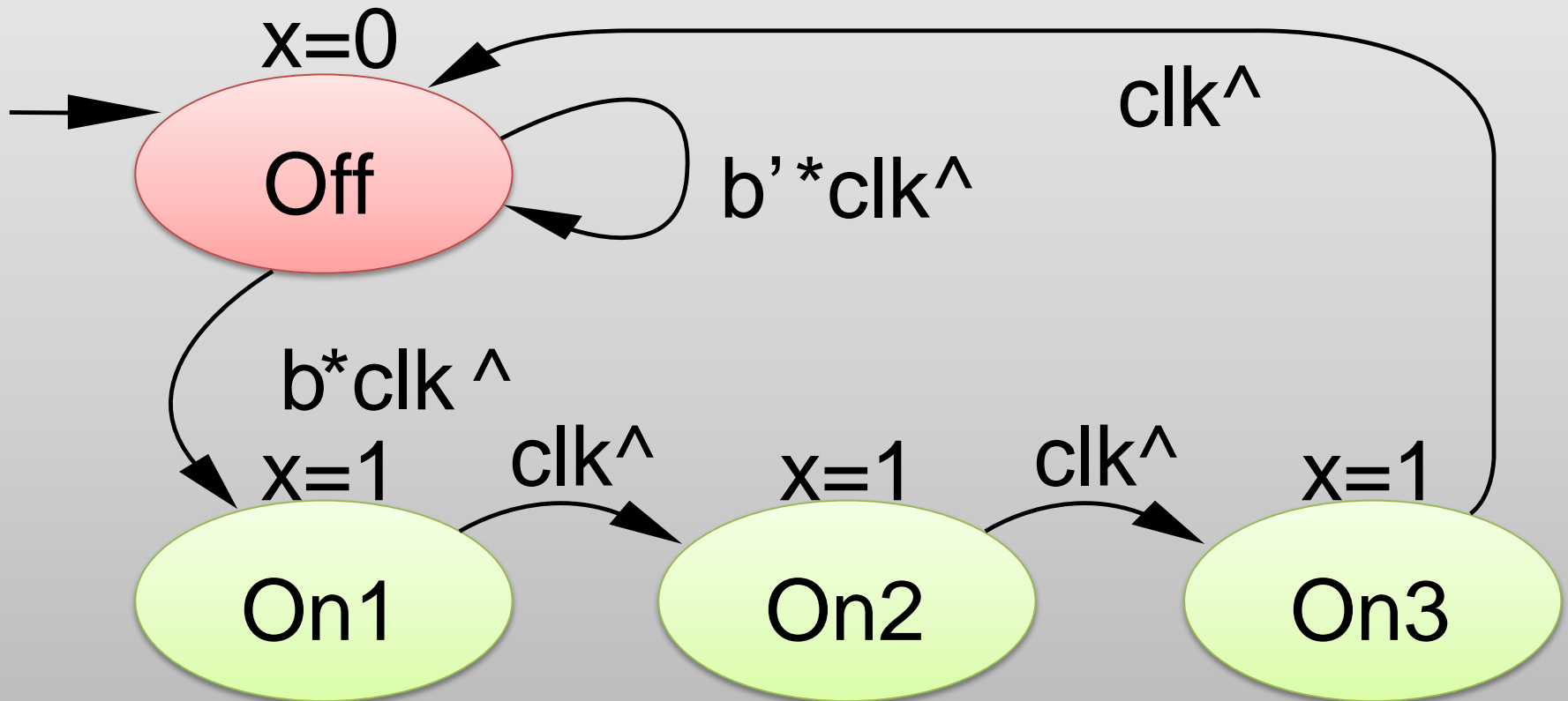

*Note: Transition with no associated condition thus transitions to next state on next clock cycle*

# FSM Simplification: Rising Clock Edges Implicit


Inputs:  $b$ ; Outputs:  $x$

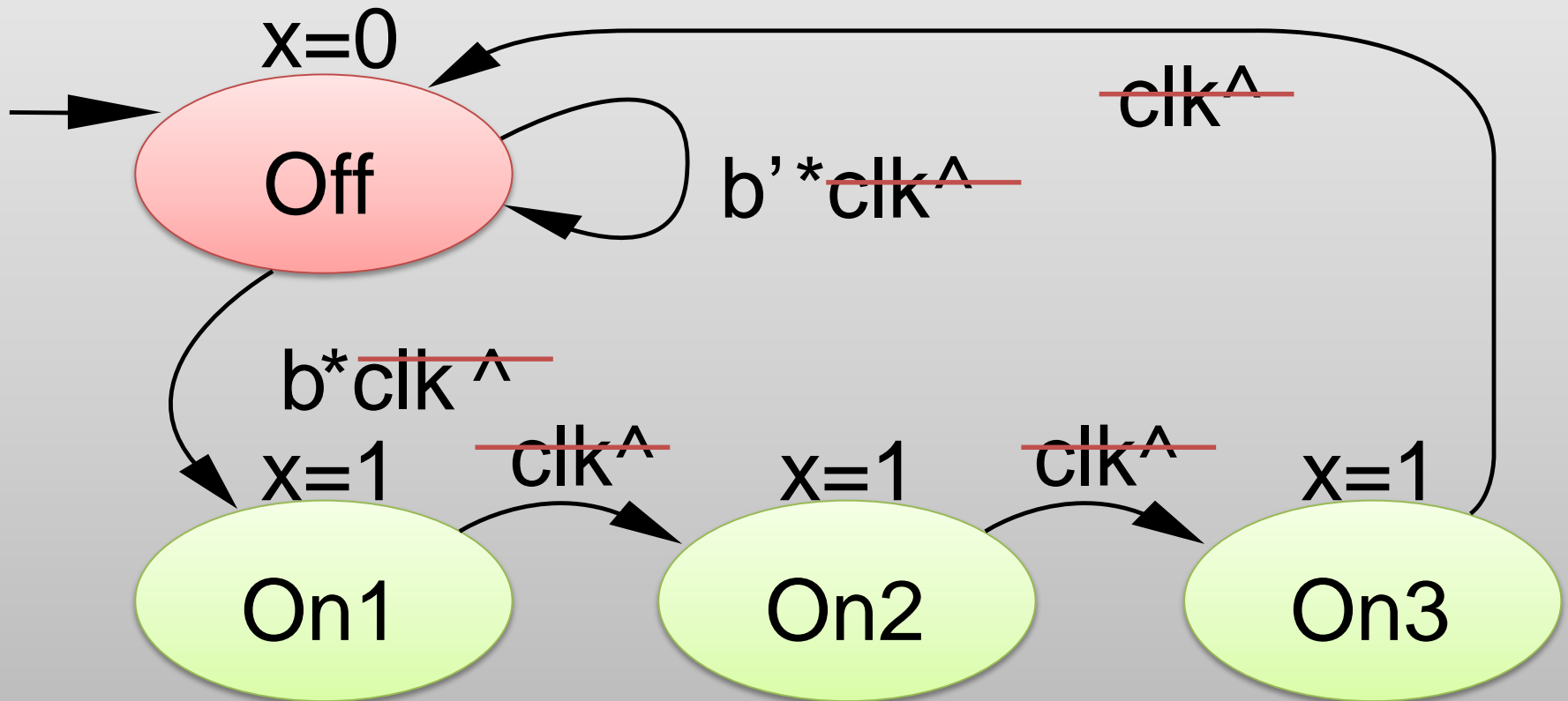

*Note: Transition with no associated condition thus transitions to next state on next clock cycle*

# FSM Simplification: Rising Clock Edges Implicit


Inputs:  $b$ ; Outputs:  $x$

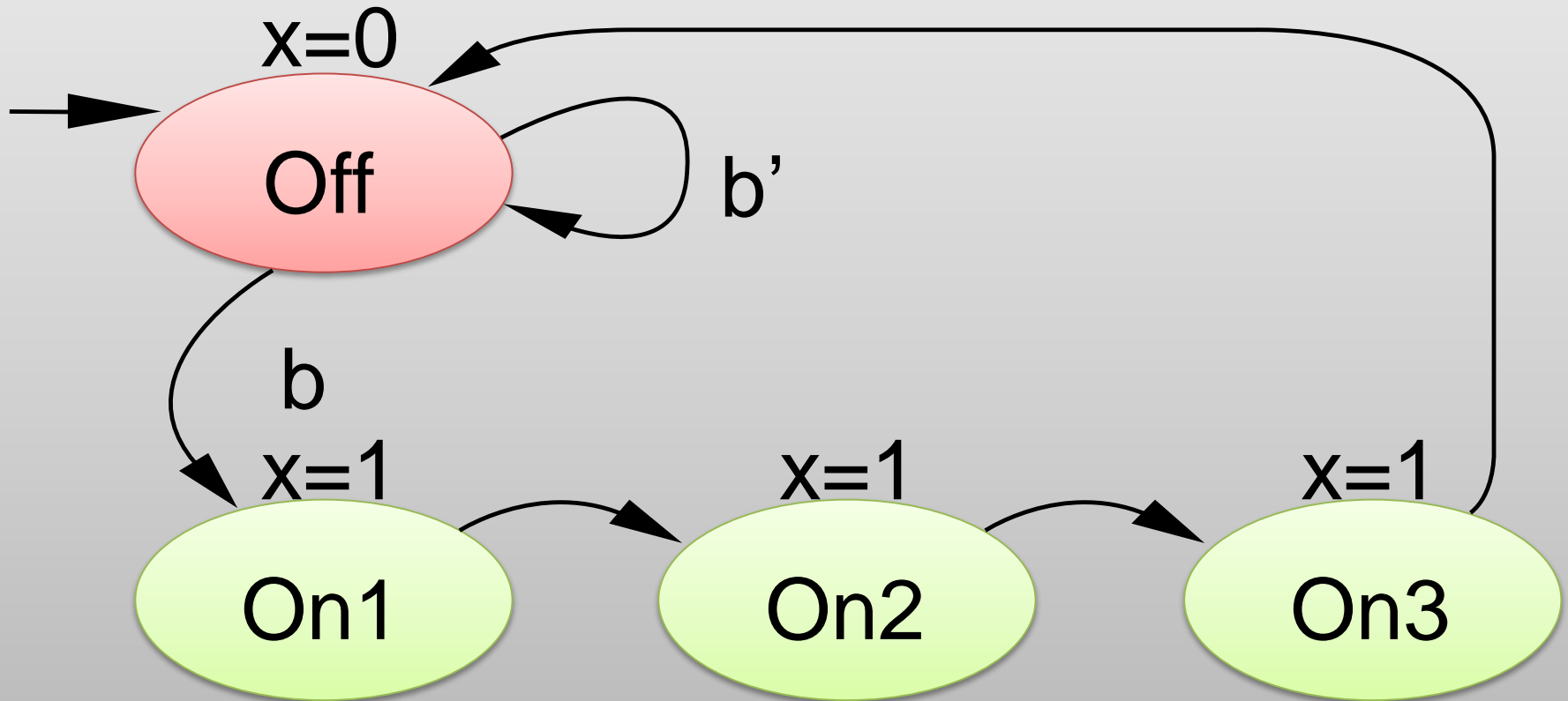

*Note: Transition with no associated condition thus transistions to next state on next clock cycle*
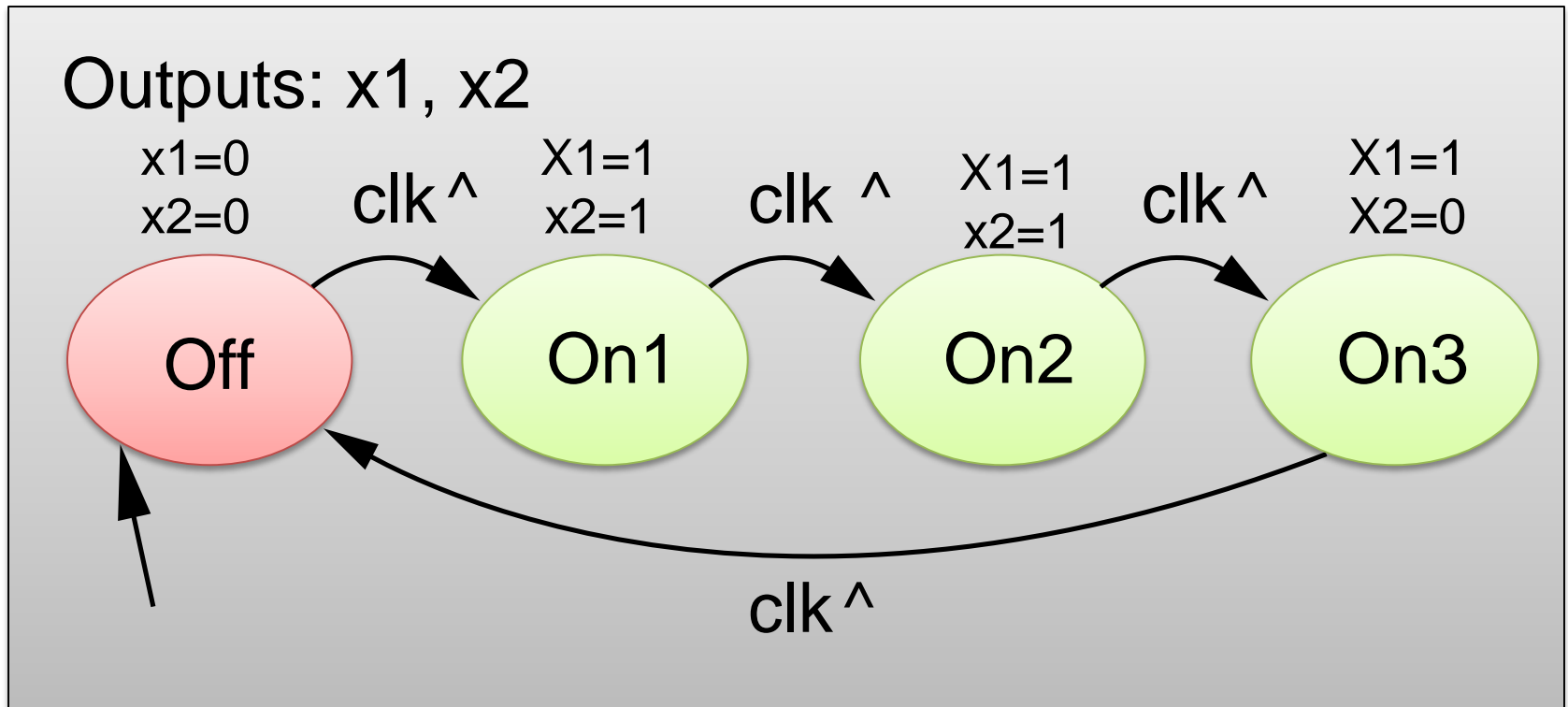
# FSM Example 4A: Sequence generator


- Generate two output sequence
  - $X1 = 01110111\dots$ repeat
  - $X2 = 01100110\dots$ repeat




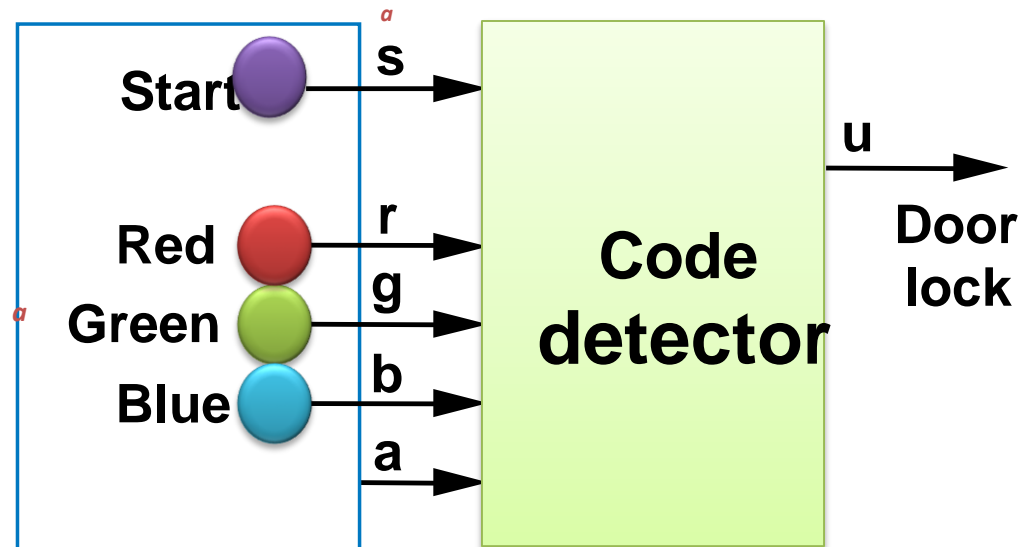
# FSM Example 5 : Code Detector


- Unlock door ( $u=1$ ) only when buttons pressed in sequence:
  - **start, then red, blue, green, red**
- Input from each button:  $s, r, g, b$ 
  - Also, output  $a$  indicates that some colored button pressed



# FSM Example 5: Code Detector

- Wait for start ( $s=1$ ) in “Wait”,
- **Once started (“Start”)**
  - If see red, go to “Red1”
  - Then, if see blue, go to “Blue”, Then, if see green, go to “Green”, Then, if see red, go to “Red2”
  - In that state, open the door ( $u=1$ )
  - Wrong button at any step, return to “Wait”


# FSM Example 5 : Code Detector

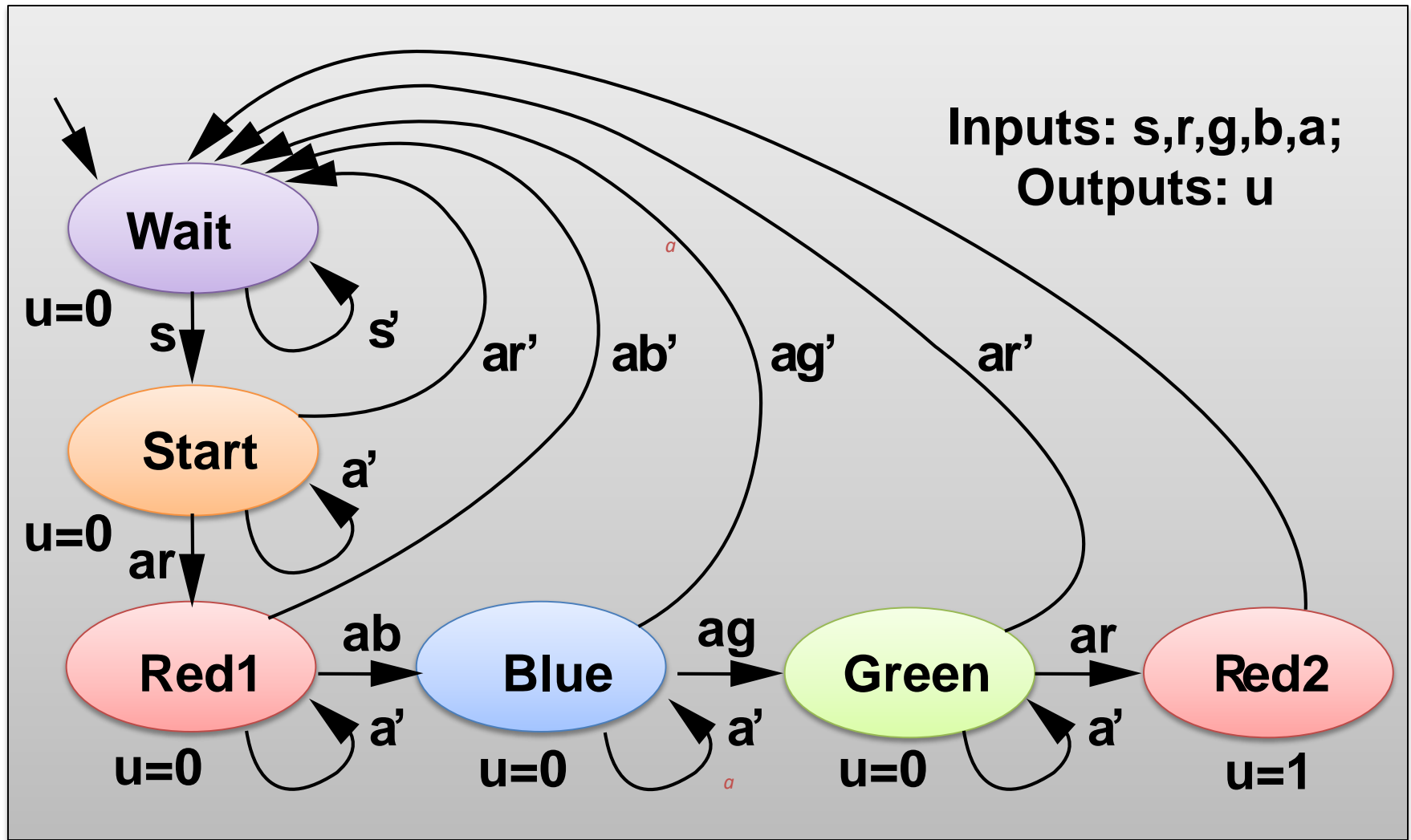

**Q: Can you trick this FSM to open the door, without knowing the code?**

**A: Yes, hold all buttons simultaneously**

# Improve FSM for Code Detector

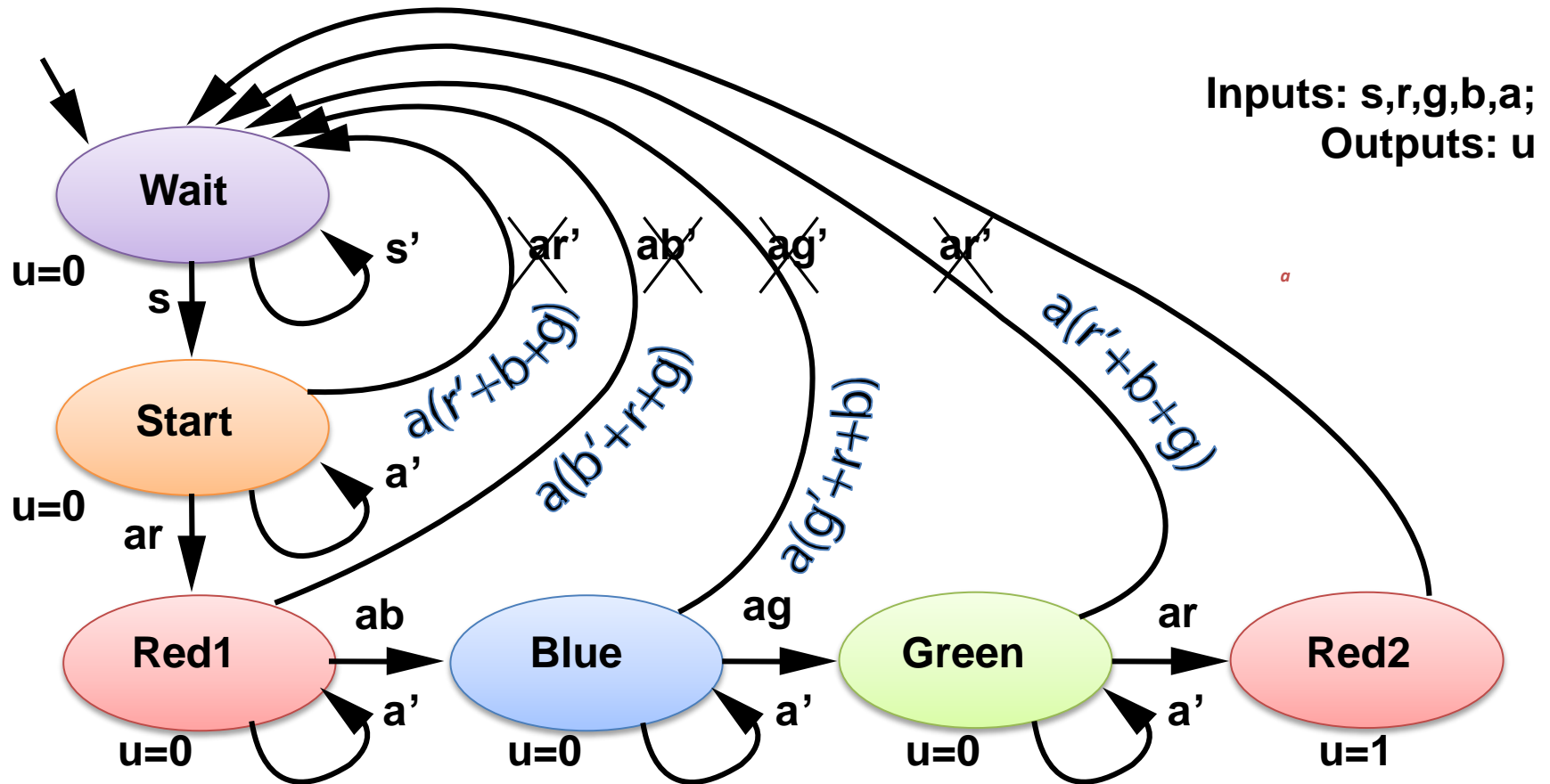

- **New transition conditions** detect if wrong button pressed, returns to “Wait”
- FSM provides formal, concrete means to accurately define desired behavior