

**Lect 11****Adder and Multiplier****CS221: Digital Design**

Dr. A. Sahu

Dept of Comp. Sc. &amp; Engg.

Indian Institute of Technology Guwahati

1


**Outline**

- Combinational Block
- Adder, Subtractor, BCD Adder
- Efficient : Adder Design
  - RCA, CS<sub>k</sub>A, CS<sub>l</sub>A, CLA
- Binary Multiplier
  - Array, Sequential, Booth
- Floating Point

2


**Adding Two One-bit Operands**

- One-bit Half Adder:

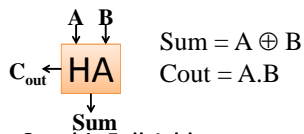

A	B	Sum	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


- One-bit Full Adder:

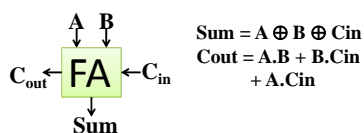


C <sub>in</sub>	A	B	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**N-Bit Ripple-Carry Adder: Series of FA Cells**


- To add two n-bit numbers

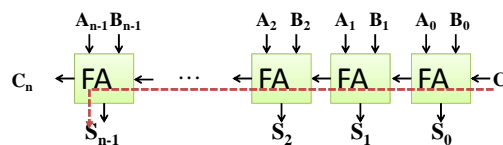

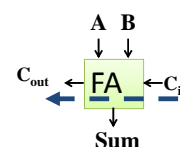
- Adder delay =  $T_c * n$
- $T_c = (C_{in} \text{ to } C_{out} \text{ delay}) \text{ of a FA}$
- Adder Area:  $N * A_{FA}$



4

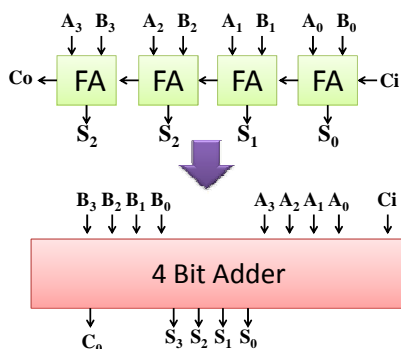
**4 bit Binary Adder**

5

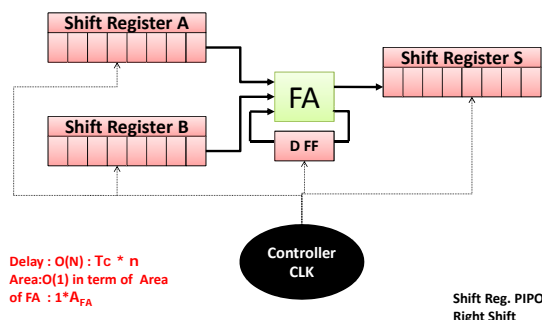**4 bit Binary Adder: Serial**

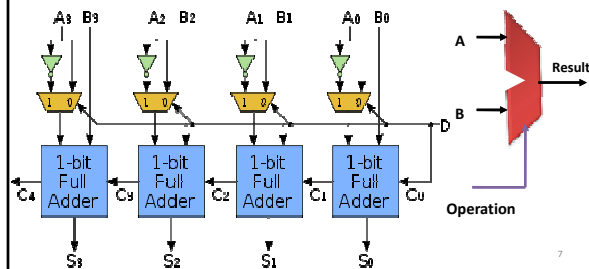
### Adder/Subtractor

- $C = B - A = B + (-A) = B + (A^b + 1)$ ,  $A^b$  is complement of A
- D is control bit: D=0/1 operation is add/sub


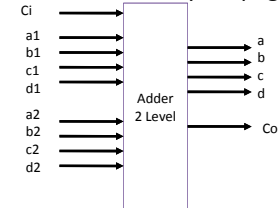
### Binary Adder (Two Level)


- Treat as 9 input & 5 output functions
- Generate Truth Table for each outputs
- Solve each function using KMAP/QM Method
- Only Two Level: No carry Propagation




### Decimal Adder

- Decimal numbers are represented with BCD code.
- When two BCD digits A and B are added
  - if  $A+B < 10$  result is a valid BCD digit
  - if  $A+B > 9$  result will not be valid BCD digit. It must be corrected by adding 6 to the result
- If  $A+B > 9$  add 6 to solve this issue


### Decimal Adder



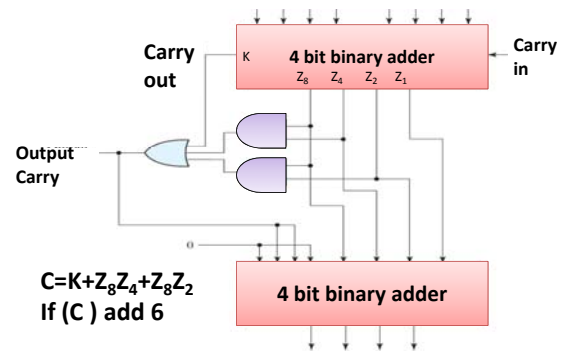


### Binary Multiplier: 2 Bits

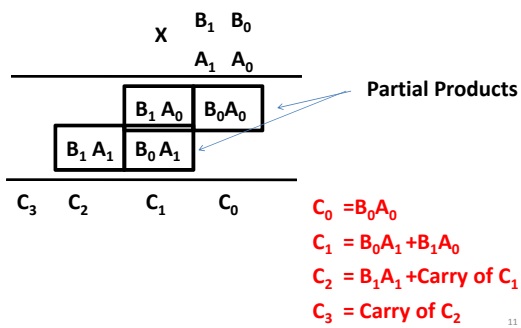

### Binary Multiplier: 2 Bits

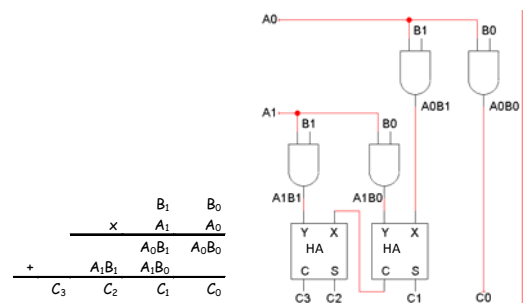

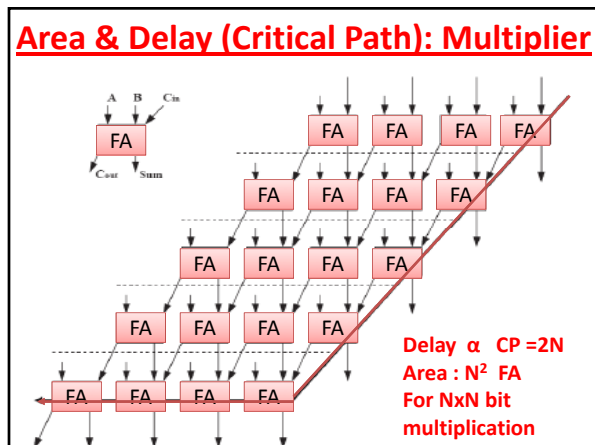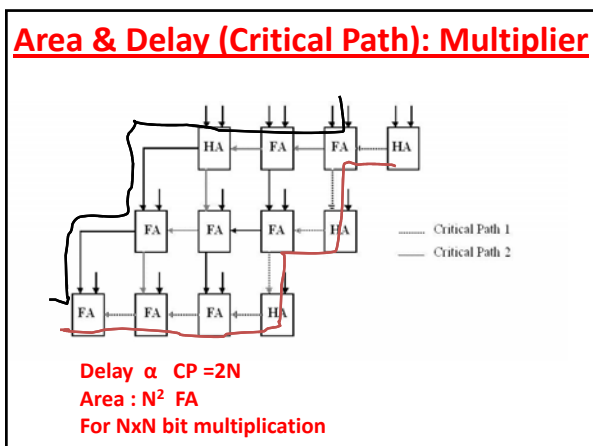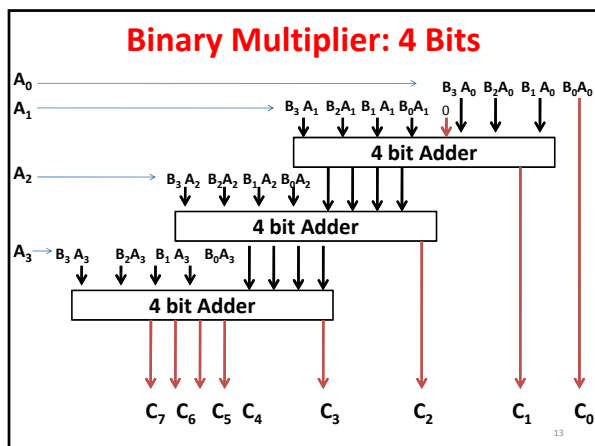


## Efficient Adder Design

### Adder Universal Use

- Adder :  $A = B + C$
- Subtractor:  $A = B + (-C)$ , 2's complement
- Compare :  $C = A > B ? 1 : 0$ ,  $(A - B > 0) ? 1 : 0$   
— Special case of compare with 0
- Multiply
- Divide
- Mod
- Floating point: Add/sub/mul...

### Adding Two One-bit Operands

- One-bit Full adder

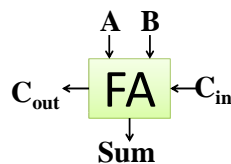

$$\text{Sum} = A \oplus B \oplus \text{Cin}$$

$$\text{Cout} = A.B + B.\text{Cin} + A.\text{Cin}$$

Cin	A	B	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

### Addition of Two N-Bit numbers

$$x + y + c_{in} = 2^n c_{out} + s$$

The solution:

$$s = (x + y + c_{in}) \bmod 2^n$$

$$c_{out} = 1 \text{ if } (x + y + c_{in}) \geq 2^n \text{ else } 0$$

19

### Example

- $011110 + 101101 = 1(x 2^6) + 001011$

- $X=30, Y=45$
- $30 + 45 = 75 = 2^6 \times 1 + 11$
- Solution
  - $S = (30+45+0) \% 2^6 = 11$
  - $C_{out} = 1 \text{ if } (30+45+0) \geq 2^6 \text{ else } 0 = 1$


### Primitive module FA

$$x_i + y_i + c_i = 2 c_{i+1} + s_i$$

with solution

- $s_i = (x_i + y_i + c_i) \bmod 2$

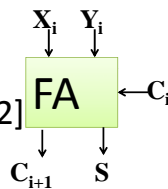
- $c_{i+1} = \text{floor} [(x_i + y_i + c_i)/2]$




21

### N-Bit Ripple-Carry Adder: Series of FA Cells

- To add two n-bit numbers

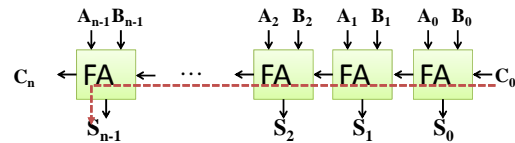

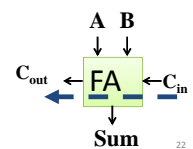
- Adder delay =  $T_c \times n$
- $T_c = (C_{in} \text{ to } C_{out} \text{ delay}) \text{ of a FA}$



22
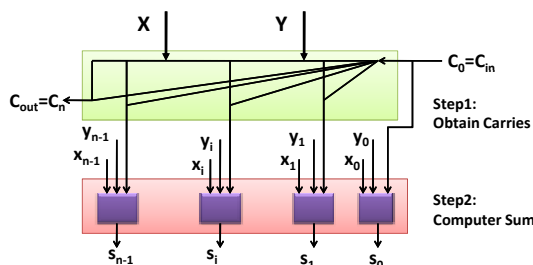
### Adder Schemes

- Step1: Obtain carries
  - (Carry at i depends on  $j < i$ ), Non-trivial to do fast
- Step2: Compute sum bits (local function)



23

### Mathematically: $C_i$ & $S_i$

- $C_i = \text{FuncC} (x_{i-1}, \dots, x_0, y_{i-1}, \dots, y_0, c_{in})$
- $S_i = \text{FuncS} (x_i, y_i, c_i)$   
 $= (x_i + y_i + c_i) \bmod 2$

24