

Lect 20 Verilog HDL

CS221: Digital Design

Dr. A. Sahu
Dept of Comp. Sc. & Engg.
Indian Institute of Technology Guwahati

9/10/2018

Outline

- HDL Programming : Verilog HDL
- HDL Rules
- HDL Module and Examples
- HDL levels : Data flow, Structural and Behavioral, UDP
- Testing and Simulation

9/10/2018

Boolean Expressions

- Use reserved word **assign**
- AND (&), OR (|) and NOT (~)
- Example:

```
// Boolean Circuit representation
module BooleanCircuit (E,F,A,B,C,D);
    output    E,F;
    input     A,B,C,D;

    assign    E= A | (B&C) | (~B&D);
    assign    F= (~B &C) | (B& ~C & ~D);
endmodule
```

10/09/2018

3

User Defined Primitives

- System primitives: **and, or, nand, xor**
- One way is to define own primitive by a Truth Table....
- Use **primitive** and **endprimitive** to create a UDP
- It is declared with the reserved word **primitive** followed by a name and port list
- One output and it must be listed first in the port listing and following the **output** declaration

10/09/2018

4

User Defined Primitives

- Any number of inputs, however the order given in the port declaration must be the same as the Table
- The table must start with the reserved word **table** and end with **endtable**
- The values of the inputs are listed in order and separated from output by : the line ends with ;

10/09/2018

5

User Defined Primitives (UDP)

```
primitive UDP_02467 (D,A,B,C);
output    D;
input     A,B,C;
// Truth Table for D= f( A, B ,C ) = Σ m(0,2,4,6,7);
table // A  B   C   :   D   // headers
    0   0   0   :   1;
    0   0   1   :   0;
    0   1   0   :   1;
    0   1   1   :   0;
    1   0   0   :   1;
    1   0   1   :   0;
    1   1   0   :   1;
    1   1   1   :   1;
endtable
endprimitive
```


10/09/2018

Calling of UDP

```
// Verilog model: Circuit instantiation of Circuit_UPD_02467
module Circuit_withUDP_02467 (e,f,a,b,c,d);
  output e,f;
  input a,b,c,d;

  UDP_02467 (e,a,b,c);


  and (f,e,d);
endmodule
```

 

10/09/2018


7

Hierarchical Design

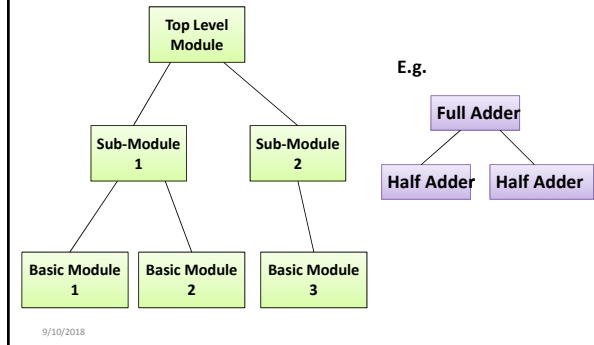

9/10/2018

Example: Half Adder

 

9/10/2018

```
module half_adder(S,C,A,B);
  output S, C;
  input A, B;

  wire S, C, A, B;

  assign S = A ^ B;
  assign C = A & B;
endmodule
```

How to build and test a module

- Construct a “test bench” for your design
 - Develop your hierarchical system within a module that has input and output ports (called “**design**” here)
 - Develop a separate module to generate tests for the module (“**test**”)
 - Connect these together within another module (“**testbench**”)

10

How to build and test a module

```
module testbench ();
  wire l, m, n;

  design d(l, m, n);
  test t(l, m);

  initial begin
    //monitor and display
    ...
  end
```

11

```
module design(a, b, c);
  input a, b;
  output c;
  ...
endmodule
```


```
module test(q, r);
  output q, r;

  initial begin
    //drive the outputs with signals
  end
```

Another view of this

- 3 chunks of verilog, one for each of:

 TESTBENCH is the final piece of hardware which connect DESIGN with TEST so the inputs generated go to the thing you want to test...



12

Verilog Examples: TB of HA

Module testAdd generated inputs for module halfAdd and displayed changes. Module halfAdd was the design

```
module tBench;
  wire su, co, a, b;
  halfAdd ad(su, co, a, b);
  testAdd tb(a, b, su, co);
endmodule
```

```
module halfAdd (sum, cOut, a, b);
  output sum, cOut;
  input a, b;
  xor #2 (sum, a, b);
  and #2 (cOut, a, b);
endmodule
```

13

Verilog Examples: TB of HA

```
module testAdd(a, b, sum, cOut);
  input sum, cOut;
  output a, b;
  reg a, b;

  initial begin
    $monitor($time, "a=%b, b=%b, sum=%b, cOut=%b",
             a, b, sum, cOut);

    a = 0; b = 0;
    #10 b = 1;
    #10 a = 1;
    #10 b = 0;
    #10 $finish;
  end
endmodule
```

14

The test module

- It's the test generator
- \$monitor
 - prints its string when executed.
 - after that, the string is printed when one of the listed values changes.
 - only one monitor can be active at any time
 - prints at end of current simulation time

15

The test module (continued)

- Function of this tester
 - at time zero, print values and set a=b=0
 - after 10 time units, set b=1
 - after another 10, set a=1
 - after another 10 set b=0
 - then another 10 and finish


```
module testAdd(a, b, sum, cOut);
  input sum, cOut;
  output a, b;
  reg a, b;

  initial begin
    $monitor($time, "a=%b,
    b=%b, sum=%b, cOut=%b",
             a, b, sum, cOut);

    a = 0; b = 0;
    #10 b = 1;
    #10 a = 1;
    #10 b = 0;
    #10 $finish;
  end
endmodule
```

16

Example: Full Adder

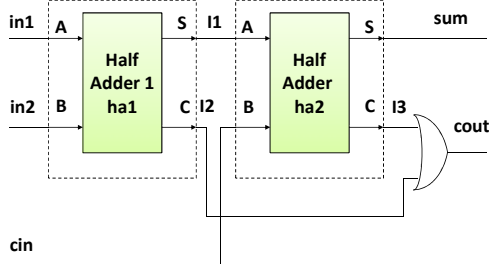

Example: Full Adder

```
module full_adder(sum, cout, in1, in2, cin);
  output sum, cout;
  input in1, in2, cin;

  wire sum, cout, in1, in2, cin;
  wire I1, I2, I3;


  half_adder ha1(I1, I2, in1, in2);
  half_adder ha2(sum, I3, I1, cin);

  assign cout = I2 || I3;
endmodule
```

Module name

Instance name


Hierarchical Names

 

Remember to use instance names,
not module names

9/10/2018

Port Assignments

 

9/10/2018

Full Adder and 4 bit adder

$$S = A \oplus B \oplus Cin \quad Cout = A.B + B.Cin + A.Cin$$

```
module FA(output S, Cout, input A,B,Cin);
  assign S=A^B^Cin;
  assign S= (A&B) | (B &Cin) | (A&Cin);
endmodule
```

```
module 4BitRCA (output[3:0] S, output C4, input[3:0] A,B,
input C0);
  wire C1, C2, C3;
  //Instantiate Chain of Full Adder
  FA FA0 (S[0], C1, A[0], B[0], C0);
  FA FA1 (S[1], C2, A[1], B[1], C1);
  FA FA2 (S[2], C3, A[2], B[2], C2);
  FA FA3 (S[3], C4, A[3], B[3], C3);
endmodule
```

Continuous Assignments

a closer look

- Syntax: `assign #del <id> = <expr>;`



- Where to write them:
 - inside a module, outside procedures
- Properties:
 - they all execute in parallel
 - are order independent
 - are continuously active

9/10/2018

Verilog HDL Models

- HDL model specifies the relationship between input signals and output signals
- HDL uses special constructs to describe hardware concurrency, parallel activity flow, time delays and waveforms
- Verilog code for a AND gate

```
module and_gate(y, x1, x2);
  input x1, x2;
  output y;

  and(y, x1, x2);
endmodule
```

23

Verilog Examples

```
module Add_half (sum, c_out, a, b);
  output sum, c_out;
  input a, b;

  wire c_out_bar;

  xor G1 (sum, a, b);
  nand G2 (c_out_bar, a, b);
  not G3 (c_out, c_out_bar);
endmodule
```

* the instance name of Verilog primitives is optional.

24

Verilog Example: behavioral model

```

module adder_4_RTL (a, b, c_in, sum, c_out);
  output [3:0]    sum;
  output         c_out;
  input [3:0]    a, b;
  input          c_in;


  assign {c_out, sum} = a + b + c_in;
endmodule

```

25

Behavioral Model - Procedures (i)

 - Procedures = sections of code that we know they execute sequentially
- Procedural statements = statements inside a procedure (they execute sequentially)
- e.g. another 2-to-1 mux implem:



9/10/2018

Behavioral Model - Procedures (ii)

- Modules can contain any number of procedures
- Procedures execute in parallel (in respect to each other)
- And can be expressed in two types of blocks:
 - **initial** → they execute only once
 - **always** → they execute for ever (until simulation finishes)

9/10/2018

“Initial” Blocks

Start execution at sim time zero and finish when their last statement executes

```

module nothing;

  initial
    $display("I'm first");

  initial begin
    #50;
    $display("Really?");
  end

endmodule

```


Will be displayed at sim time 0

Will be displayed at sim time 50

9/10/2018

“Always” Blocks

 - Start execution at sim time zero and continue until sim finishes



9/10/2018

Events (i)

```

always @(signal1 or signal2 or ..)
begin
  ..
end

```

execution triggers every time any signal changes

```

always @(posedge clk)
begin
  ..
end

```

execution triggers every time clk changes from 0 to 1

```

always @(negedge clk)
begin
  ..
end

```

execution triggers every time clk changes from 1 to 0

Examples: always@

```

module half_adder(S, C, A, B);
  output      S, C;
  input       A, B;

  reg         S, C;
  wire        A, B;

  always @(A or B) begin
    S = A ^ B;
    C = A && B;
  end

endmodule

```

9/10/2018

Events (ii) : wait

```

always begin
  wait (ctrl)
  #10 cnt = cnt + 1;
  #10 cnt2 = cnt2 + 2;
end

```

execution loops every
time ctrl = 1 (level sensitive
timing control)

9/10/2018


Timing (i)

```

initial begin
  #5 c = 1;
  #5 b = 0;
  #5 d = c;
end

```

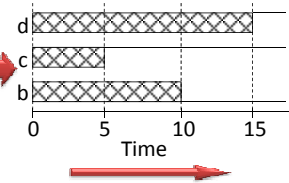Each assignment is
blocked by its previous one



9/10/2018


Timing (ii)

```

initial begin
  fork
    #5 c = 1;
    #5 b = 0;
    #5 d = c;
  join
end

```

Assignments are
not blocked here

 

9/10/2018

Procedural Statements: if

```

module mux4_1(out, in, sel);
  output      out;
  input[3:0]  in;
  input[1:0]  sel;

  reg         out;
  wire [3:0]  in;
  wire [1:0]  sel;

  always @(in or sel)
    if (sel == 0)
      out = in[0];
    else if (sel == 1)
      out = in[1];
    else if (sel == 2)
      out = in[2];
    else
      out = in[3];
endmodule

```

Procedural Statements: case

```

module mux4_1(out, in, sel);
  output      out;
  input[3:0]  in;
  input[1:0]  sel;

  reg         out;
  wire [3:0]  in;
  wire [1:0]  sel;

  always @(in or sel)
    case (sel)
      0: out = in[0];
      1: out = in[1];
      2: out = in[2];
      3: out = in[3];
    endcase
endmodule

```

Procedural Statements: for

```

module count(Y, start);
output [3:0] Y;
input      start;

reg [3:0]    Y;
wire        start;
integer      i;

initial
    Y = 0;

always @(posedge start)
    for (i = 0; i < 3; i = i + 1)
        #10 Y = Y + 1;
endmodule

```

9/10/2018

Procedural Statements: while

```

module count(Y, start);
output [3:0] Y;
input      start;

reg [3:0]    Y;
wire        start; integer i;

initial
    Y = 0;
always @(posedge start)
    i = 0;
    while (i < 3) begin
        #10 Y = Y + 1;
        i = i + 1;
    end
end
endmodule

```

9/10/2018

Procedural Statements: repeat

```

module count(Y, start);
output [3:0] Y;
input      start;

reg [3:0]    Y;
wire        start;
integer      i;

initial
    Y = 0;

always @(posedge start)
    repeat (4) #10 Y = Y + 1;
endmodule

```

9/10/2018

Procedural Statements: forever

forever stmt;

Executes until sim
finishes

//clock generation in test
modules

```

module test;
reg clk;
initial begin
    clk = 0;
    forever #10 clk = ~clk;
end

other_module1 o1(clk, ..);
other_module2 o2(..,
clk,..);
endmodule


```

$T_{clk} = 20$ time units

9/10/2018

Mixed Model

 Code contains various both structure and behavioral styles



```

module simple(Y, c, clk, res);
output Y;
input c, clk, res;

reg Y;
wire c, clk, res, n;

not(n, c); // gate-level

always @(res or posedge clk)
    if (res)
        Y = 0;
    else
        Y = n;
endmodule

```

9/10/2018

System Tasks

Always written inside procedures

- **\$display**("..", arg2, arg3, ..);
– much like printf(), displays formatted string in std output when encountered
- **\$monitor**("..", arg2, arg3, ..);
– \$display(), but .. displays string each time any of arg2, arg3, .. Changes
- **\$stop**; → suspends sim when encountered
- **\$finish**; → finishes sim when encountered

9/10/2018

System Tasks

Always written inside procedures

- **\$fopen**("filename");
 - returns file descriptor (integer);
 - Then you can use **\$fdisplay**(fd, "..", arg2, arg3, ..); or **\$fmonitor**(fd, "..", arg2, arg3, ..); to write to file
- **\$fclose**(fd); → closes file
- **\$random**(seed); → returns random integer;
 - integer as a seed

9/10/2018

\$display & \$monitor string format

Format	Display
%d or %D	Display variable in decimal
%b or %B	Display variable in binary
%s or %S	Display string
%h or %H	Display variable in hex
%c or %C	Display ASCII character
%m or %M	Display hierarchical name
%v or %V	Display strength
%o or %O	Display variable in octal
%t or %T	Display in current time format
%e or %E	Display real number in scientific format
%f or %F	Display real number in decimal format
%g or %G	Display scientific or decimal, whichever is shorter


9/10/2018

Variety of Coding Style in Verilog

4x1 Mux Example

9/10/2018

4x1 Multiplexer

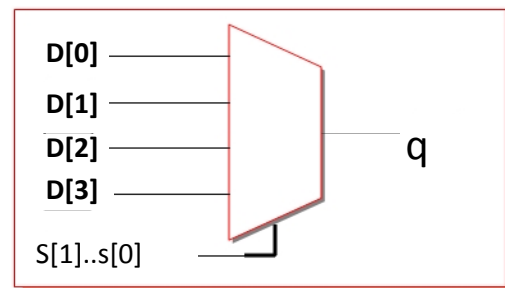

9/10/2018

4x1 Multiplexer : structural


```

module mux1( S, d, q );
  input[1:0] S;
  input[3:0] d;
  output q;

  wire q, q1, q2, q3, q4, NS0, NS1;
  wire[1:0] S;
  wire[3:0] d;

  not n1( NS0, S[0] );
  not n2( NS1, S[1] );
  and a1( q1, NS0, NS1, d[0] );
  and a2( q2, S[0], NS1, d[1] );
  and a3( q3, NS0, S[1], d[2] );
  and a4( q4, S[0], S[1], d[3] );
  or o1( q, q1, q2, q3, q4 );
endmodule

```

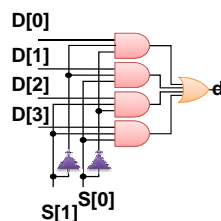

4x1 Multiplexer : Data Flow


```

module mux1( S, d, q );
  input[1:0] S;
  input[3:0] d;
  output q;

  wire q;
  wire[1:0] S;
  wire[3:0] d;

  assign q = d[S];
endmodule

```

 

4x1 Multiplexer : Data Flow

```

module mux1( S, d, q );
  input[1:0] S;
  input[3:0] d;
  output q;

```

```

  wire q;

```

```

  wire[1:0] S;

```

```

  wire[3:0] d;

```

```


  assign q = (S == 0)? d[0] : ( S == 1 )? d[1]
    : ( S == 2 )? d[2] : d[3];

```

```

endmodule

```

 **4x1 Multiplexer: Behav-Data Flow**

```

module mux1( S, d, q );
  input[1:0] S;
  input[3:0] d;
  output q;

```

```

  reg q;

```

```

  wire[1:0] S;

```

```

  wire[3:0] d;

```

```

always @(d or S)

```

```

begin

```

```

  q = ( ~S[0] & ~S[1] & d[0] ) |

```

```

    ( S[0] & ~S[1] & d[1] ) |

```

```

    ( ~S[0] & S[1] & d[2] ) |

```

```

    ( S[0] & S[1] & d[3] );

```

```


end

```

```

endmodule

```

 **4x1 Multiplexer**

```

module mux1( S, d, q );
  input[1:0] S;
  input[3:0] d;
  output q;

```

```

  reg q;

```

```

  wire[1:0] S;

```

```

  wire[3:0] d;

```

```

always @(d or S)

```

```


  q = d[select];

```

```

endmodule

```

 **4x1 Multiplexer**

```

module mux1( S, d, q );
  input[1:0] S;
  input[3:0] d;
  output q;

```

```

  reg q;

```

```

  wire[1:0] S;

```

```

  wire[3:0] d;

```

```

always @(d or S)

```

```

begin

```

```

  if( S == 0) q = d[0];

```

```

  if( S == 1) q = d[1];

```

```

  if( S == 2) q = d[2];

```

```


  if( S == 3) q = d[3];

```

```

endmodule

```

 **4x1 Multiplexer**

```

module mux1( S, d, q );
  input[1:0] S;
  input[3:0] d;
  output q;

```

```

  reg q;

```

```

  wire[1:0] S;

```

```

  wire[3:0] d;

```

```

always @(d or S)

```

```

begin case ( S )

```

```

  0 : q = d[0];

```

```

  1 : q = d[1];

```

```

  2 : q = d[2];

```

```

  3 : q = d[3];

```

```


endcase

```

```

endmodule

```

 **2x1 Mux using UDP**

```

primitive Mux (y, a, b, sel); // combinational UDP

```

```

  output y;

```

```

  input a, b, sel;

```

```

  table // a b sel : y

```

```

    0 ? 0 : 0;

```

```

    1 ? 0 : 1;

```

```

    ? 0 1 : 0;

```

```

    ? 1 1 : 1;

```

```

endtable

```

```

endprimitive

```

9/10/2018