

CS221: Digital Design

<http://jatinga.iitg.ernet.in/~asahu/cs221>

FSM: Optimization and State Encoding

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

Outline

- FSM State Optimization : RM and IC
- FSM State Encoding
- FSM + Data Path
- ASM

FSM State Minimization

FSM State Minimization

- Minimizing number of state reduce
 - Requirement of bigger size state register
 - Possibly reduce the CCC

Some Definitions

- **State Equivalence:** $S1$ and $S2$ are equivalent if for every input sequence applied to machine goes to same NS and Output
 - If $S1(t+1)=S2(t+1)$ and $Z1=Z2$ then $S1=S2$
- **Distinguishable States:** Two states $S1$ and $S2$ are Distinguishable iff there exist at least one finite input sequence which produce different outputs from $S1$ and $S2$

Methods

- Row Matching Method or Partitioning Method
 - Completely specified machine (n^2 edges)
 - Partially specified machine
- Implication Chart Method

Implication Chart Methods

FSM Reduction: Implication Chart

Method

Problem:



Single input X, Single output Z

Output a 1 whenever the serial sequence 010 or 110 has been observed at the inputs

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S_0	S_0	0	0
01	S_4	S_0	S_0	1	0
10	S_5	S_0	S_0	0	0
11	S_6	S_0	S_0	1	0

Implication Chart Method

  Enumerate all possible combinations of states taken two at a time



Naive Data Structure:

X_{ij} will be the same as X_{ji}

Also, can eliminate the diagonal

Implication Chart Method

Filling in the Implication Chart

Entry X_{ij} — Row is S_i , Column is S_j


S_i is equivalent to S_j if outputs are the same and next states are equivalent

X_{ij} contains the next states of S_i , S_j which must be equivalent if S_i and S_j are equivalent

If S_i , S_j have different output behavior, then X_{ij} is crossed out

Implication Chart Method

 If S_i, S_j have different output behavior, then X_{ij} is crossed out



Starting Implication Chart


Input	P State	NS		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S_0	S_0	0	0
01	S_4	S_0	S_0	1	0
10	S_5	S_0	S_0	0	0
11	S_6	S_0	S_0	1 ₁₁	0

Implication Chart Method

If S_i, S_j have different output behavior,
then X_{ij} is crossed out

S_4 have different out put behavior with
 S_0, S_1, S_2, S_3, S_5

 
S_6 have different out put behavior with
 S_0, S_1, S_2, S_3, S_5



Starting Implication Chart

Input	P State	NS		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S_0	S_0	0	0
01	S_4	S_0	S_0	1	0
10	S_5	S_0	S_0	0	0
11	S_6	S_0	S_0	1 ₁₂	0

Implication Chart Method

 


Fill other S_{ij} Based on Next State Transaction

S_0 : S_1, S_2 when $X=0, 1$

S_1 : S_3, S_4 when $X=0, 1$

		NS		Output	
Input	P State	$X=0$	$X=1$	$X=0$	$X=1$
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S_0	S_0	0	0
01	S_4	S_0	S_0	1	0
10	S_5	S_0	S_0	0	0
11	S_6	S_0	S_0	1 ¹³	0

Implication Chart Method

 


Starting Implication Chart

Fill others S_{ij} Based on Next State Transaction

Input	P State	NS		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S_0	S_0	0	0
01	S_4	S_0	S_0	1	0
10	S_5	S_0	S_0	0	0
11	S_6	S_0	S_0	1 <small>14</small>	0

Implication Chart Method

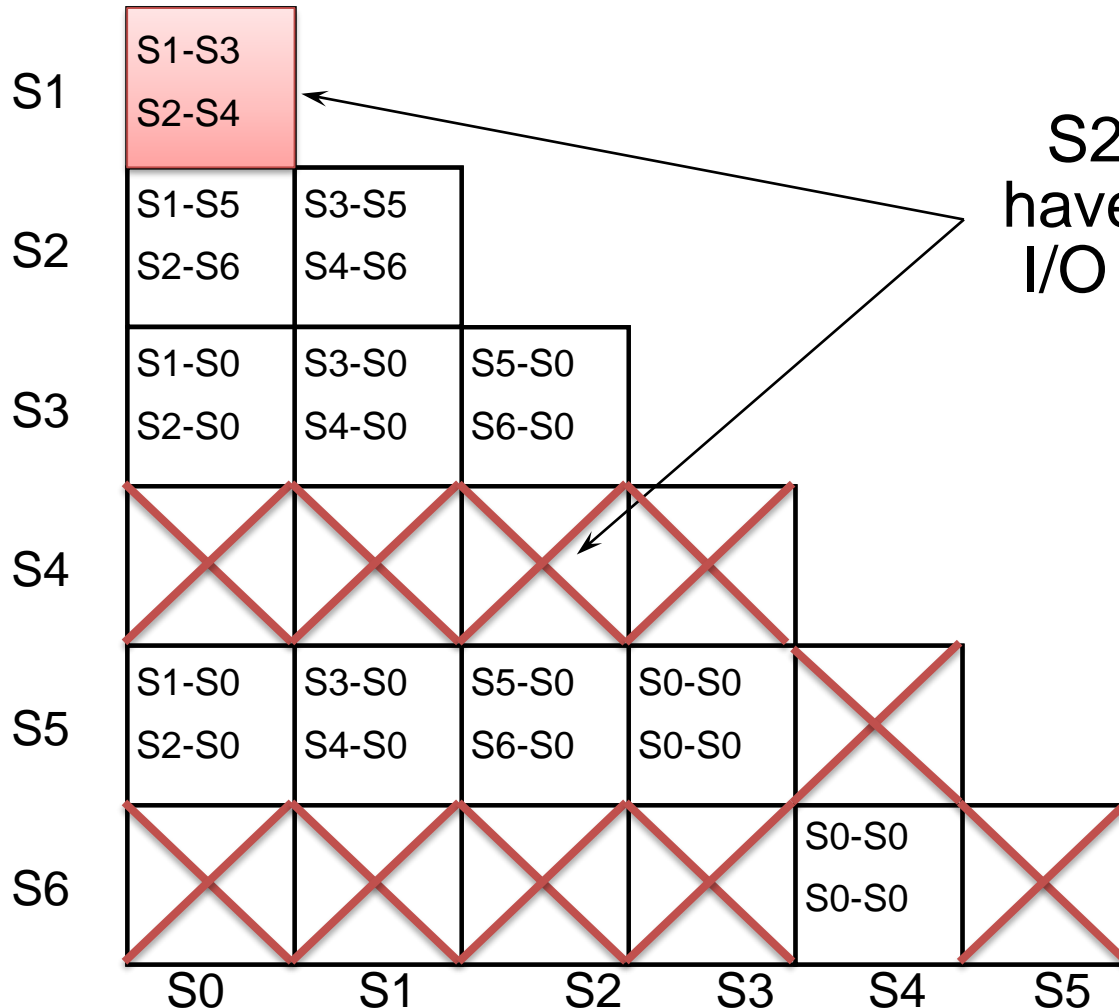


S2 and S4
have different
I/O behavior

This implies that
S1 and S0 cannot
be combined

Marked with Cross

Implication Chart Method

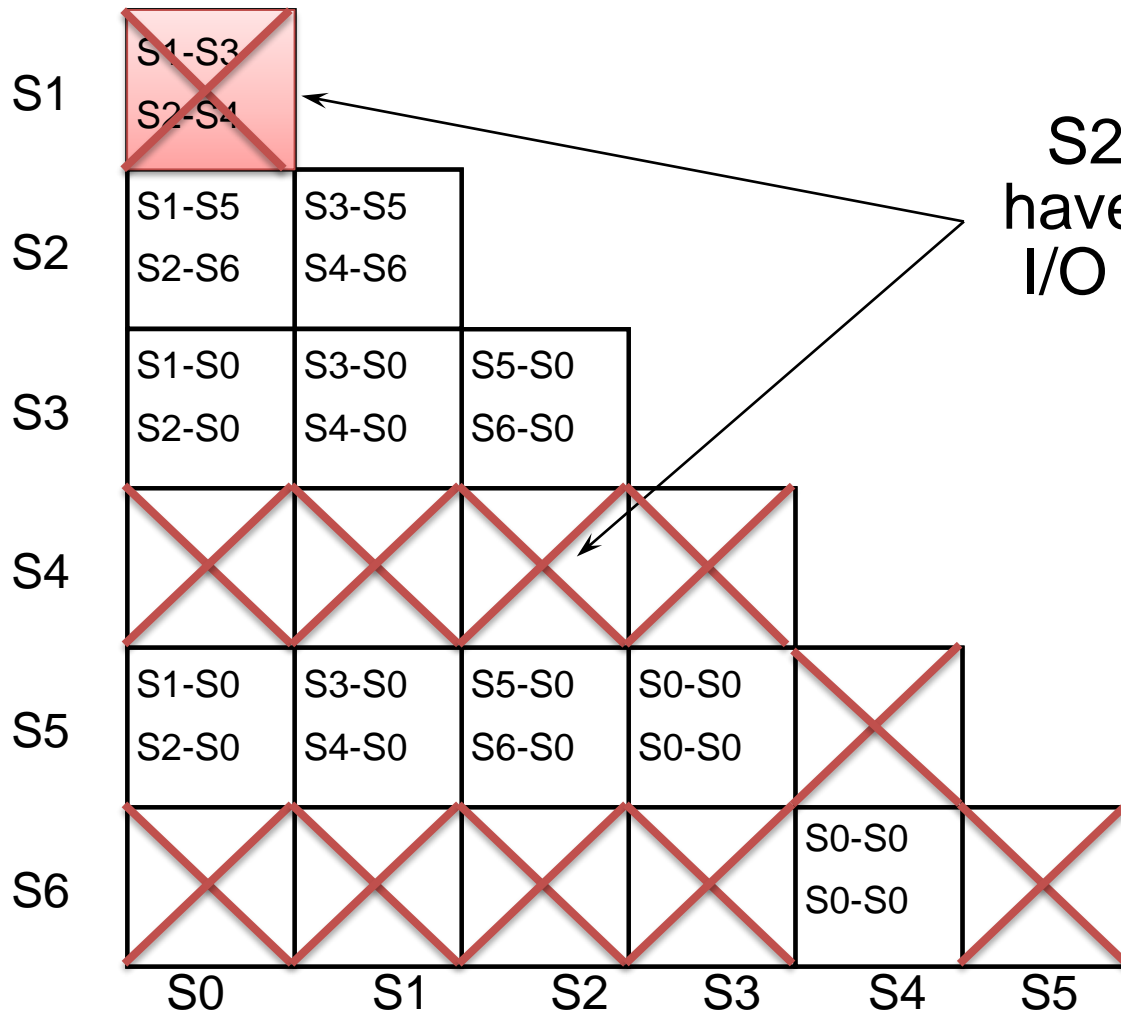


S2 and S4
have different
I/O behavior

This implies that
S1 and S0 cannot
be combined

Marked with Cross

Implication Chart Method

 


S2 and S6
have different
I/O behavior

This implies that
S1 and S0 cannot
be combined

Marked with Cross

Implication Chart Method

 


S2 and S6
have different
I/O behavior


This implies that
S2 and S0 cannot
be combined

Marked with Cross

Implication Chart Method

 


Implication Chart Method

 

S1S0 is already crossed

So S3S0


Implication Chart Method

 

S4S0 is already crossed

So S3S1


Implication Chart Method

 

S6S0 is already crossed

So S3S2


Implication Chart Method

 

S2S0 is already crossed


So S5S0

Implication Chart Method

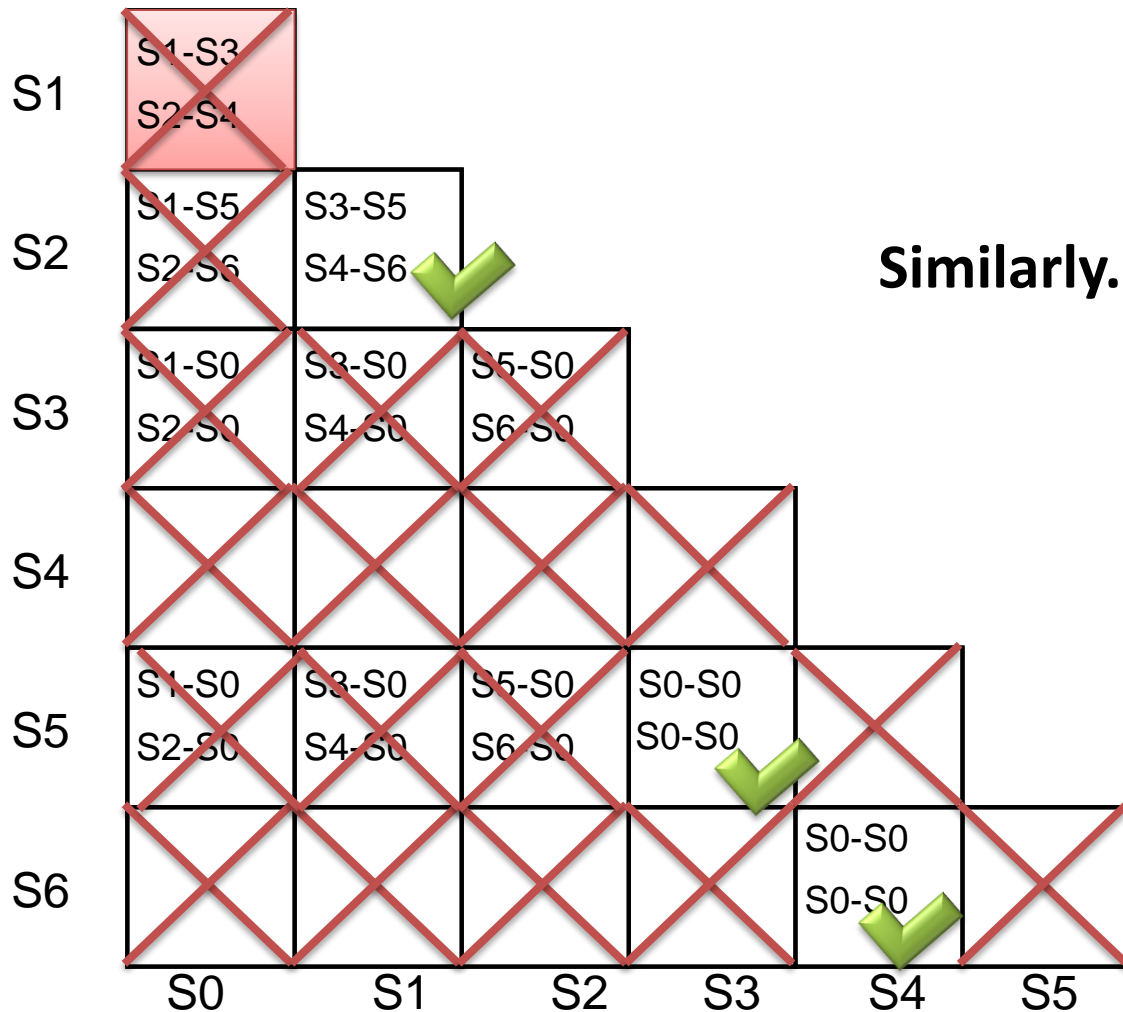

Second Pass Adds No New Information


Implication Chart Method

 

Similarly..

Second Pass Adds No New Information

Implication Chart Method

 


S3 and S5 are equivalent
S4 and S6 are equivalent
S1 and S2 are equivalent

Second Pass Adds No New Information

Final : Reduce State Table

- Reduces State table

Input	P State	NS		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S_0	S_0	0	0
01	S_4	S_0	S_0	1	0
10	S_5	S_0	S_0	0	0
11	S_6	S_0	S_0	1	0

 

Input	PS	NS		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1'	S_1'	0	0
0 or 1	S_1'	S_3'	S_4'	0	0
00 or 10	S_3'	S_0	S_0	0	0
01 or 11	S_4'	S_0	S_0	1	0

State Encoding/Assignment

State assignment

- Since we don't care about the actual flip-flop values for each state we can assign each state to any binary number we like **as long as** each state is assigned a unique binary number
- Suppose a FSM have 5 states
- If we use 3 bits to encode the 5 states, we have

$$\binom{8}{5} = \frac{8!}{5!(8-5)!}$$

possible encodings

State assignment

state	Encoding 1 (binary)	Encoding 2 (Gray)	Encoding 3
a	000	000	000
b	001	001	100
c	010	011	010
d	011	010	101
e	100	110	011

State Encoding

- Hamming/Edit Distance
 - $HD(0000,0100)=1$, $HD(0011,1100)=4$,
 $HD(1010,1111)=2$
- Binary and Gray encoding use the minimum number of bits for state register
- Gray and Johnson code: Two adjacent codes differ by only one bit
 - Reduce simultaneous switching
 - Reduce crosstalk, Reduce glitch

One-hot encoding

- One flip-flop per state encoding
- Leads to greater number of flip-flops than binary encoding but possibly to simpler o/p logic