

Lect 10**Combinational Block design****CS221: Digital Design**

Dr. A. Sahu
Dept of Comp. Sc. & Engg.
Indian Institute of Technology Guwahati

1

Outline

- Combinational Block
- Encoder, Priority Encoder
 - Decoder: N to 2^N , Encoder: 2^N to N
 - Decoder : Output selector
- Multiplexor: The input selector.....
 - 2^N to 1, N select line
- Adder, Subtractor, BCD Adder
- Binary Multiplier
- Other Encoders

2


Study of Components

- Decoder, Encoder
- Multiplexor
- Logic Implementation Using MUX & Decoder
- Mux: 7 Segment Display
- 4 Bit Adder
- N- Bit Adder

3

Multiple-Output Circuits

- Many circuits have more than one output
- Can give each a separate circuit, or can share gates
- Ex: $F = ab + c'$, $G = ab + bc$

 

Option 1: Separate circuits

Option 2: Shared gates

4


Decoder

- Reception counter : When you reach a Academic Institute
 - Receptionist Ask: Which Dept to Go ?
 - Customer : CSE
 - Receptionist Redirect you to some building according to your Answer. == > Go to Core II
- Decoder : knows what to do with this: Decode
- Digital Case: == > N input: 2^N output
- Memory Addressing
 - Address to a particular location

5

Decoders

 
- **Decoder:** Popular combinational logic building block, in addition to logic gates
 - Converts input binary number to one high output
- 2-input decoder: four possible input binary numbers
 - So has four outputs, one for each possible input binary number




6

Decoders and Muxes

 - Internal design
 - AND gate for each output to detect input combination
- Decoder with enable e
 - Outputs all 0 if e=0, Regular behavior if e=1
- n-input decoder: 2^n outputs



 4-to-16 Decoder using two 3-to-8 Decoders





Boolean Function Implementation using Decoders

- As Decoder covers all the Minterms
- Using a n-to- 2^n decoder and OR gates any functions of n variables can be implemented.
- Example: Full Adder

$$S(x,y,z) = \Sigma(1,2,4,7), \quad C(x,y,z) = \Sigma(3,5,6,7)$$
- Functions S and C can be implemented using a 3-to-8 decoder and two 4-input OR gates

Decoder: Covers All Minterms

Implementation of S and C

 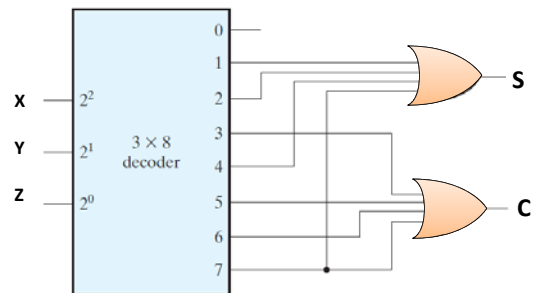

Activation of LEDs


$$F_a(W,X,Y,Z) = \Sigma m(0,2,3,5,6,7,8,9) + \Sigma d(10,11,12,13,14,15)$$

- | | |
|------------------|--------------------|
| • 0: a,b,c,d,e,f | • 5: a,f,g,c,d |
| • 1: b,c | • 6: a,f,g,c,d,e |
| • 2: a,b,g,e,d | • 7: a,b,c |
| • 3: a,b,g,c,d | • 8: a,b,c,d,e,f,g |
| • 4: f,g,b,c | • 9: a,b,c,d,f,g |

11


BCD to 7 Segment Display

 - BCD are 4 bit
- Design a decoder to drive 7 segment LED




12

 BCD to 7 Segment Decoder using 4x16 Encoder



13

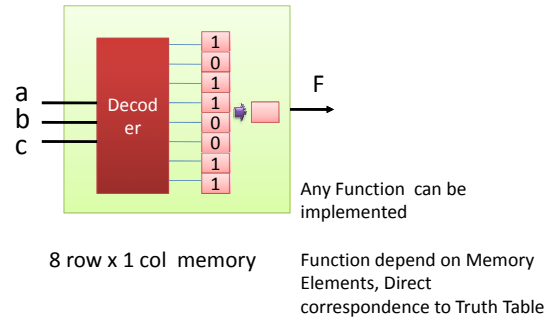Configurable Function using Decoder & Memory



14

Encoders

- A digital circuit perform the inverse operation of Decoder
- 4x2 Encoder : 4 input lines A, B, C, D and two output lines X, Y

A	B	C	D	X	Y
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

$$X = A'B'CD' + A'B'C'D$$

$$= A'B'(CD' + C'D)$$

$$Y = A'BC'D' + A'B'C'D$$

$$= A'C'(BD' + B'D)$$

$$X = C + D$$

$$Y = B + D$$

15

Priority Encoders

- Encoder with priority function
- Two or more input is 1 at the same time: input with highest priority will take precedence
- When all the input are 0 it is invalid : V=0

A	B	C	D	X	Y	V
0	0	0	0	0	0	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

$$X = C + D$$

$$Y = D + BC' \quad // \text{mistake in class is } \Rightarrow \text{corrected...}$$

$$V = A + B + C + D$$


16

Multiplexor (Mux)


- Multiplex: Cinema, TDM, High BW
- Mux: Another popular combinational building block
 - Routes one of its N data inputs to its one output, based on binary value of select inputs
 - 4 input mux \rightarrow needs 2 select inputs to indicate which input to route through
 - 8 input mux \rightarrow 3 select inputs
 - N inputs $\rightarrow \log_2(N)$ selects

Multiplexor (Mux)

 
- Mux: Another popular combinational building block
 - Like a railyard switch




Mux Internal Design

 


Mux Internal Design

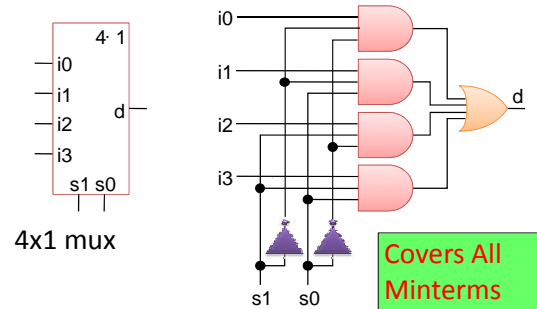

Muxes Commonly Together -- N-bit

 


Implementing logic Function using MUX

 

Implementing 3 Inputs Logic Function using 4x1 MUX

$$F(A, B, C) = \sum m(1,2,6,7)$$

A	B	C	F	F
0	0	0	0	C
0	0	1	1	C'
0	1	0	1	C'
0	1	1	0	
1	0	0	0	0
1	0	1	0	
1	1	0	1	1
1	1	1	1	

 

Implementing 5 Inputs Logic Function using two 16x1 MUX

